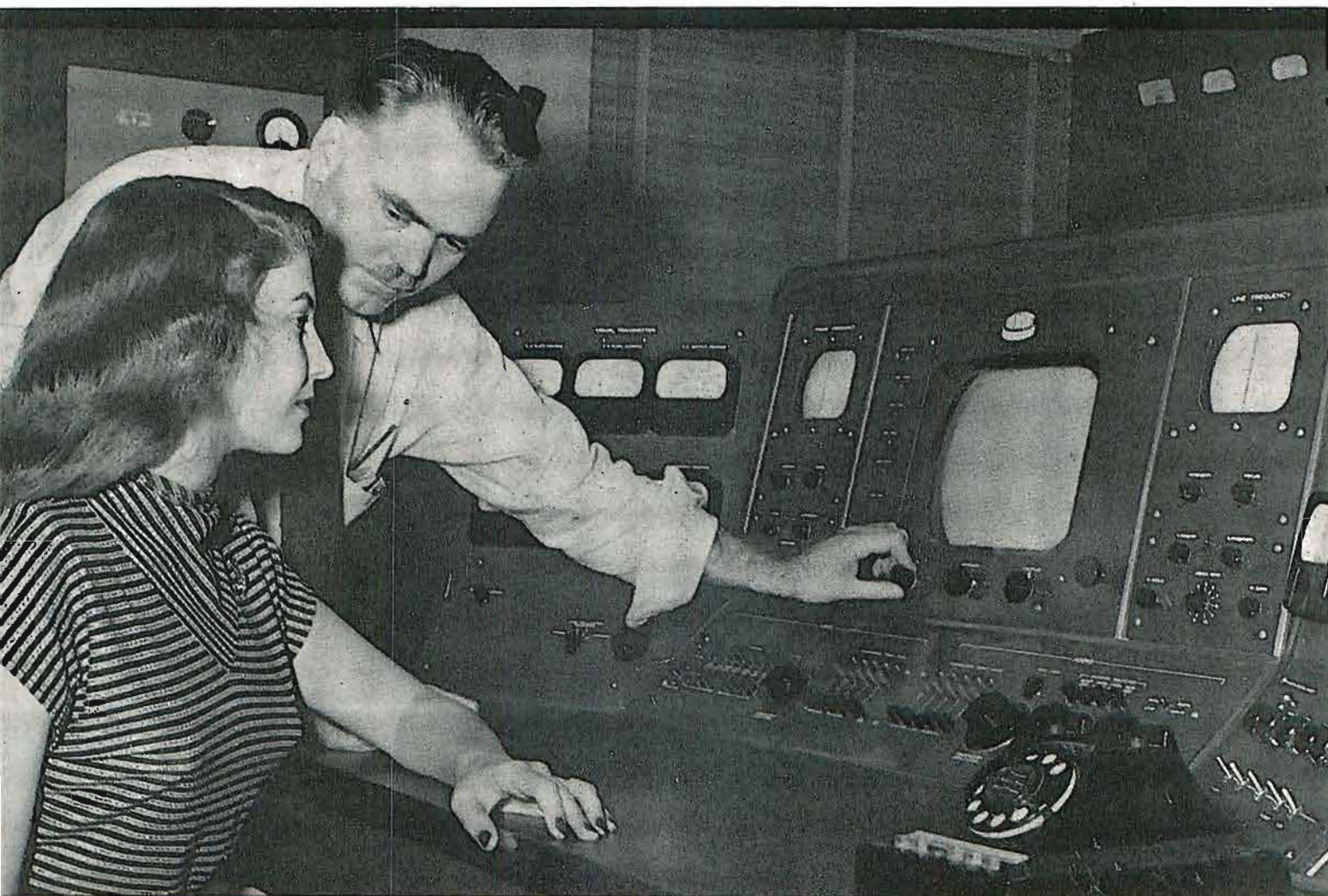


COMMUNICATIONS

INCLUDING "RADIO ENGINEERING" AND "TELEVISION ENGINEERING"



NOVEMBER

- ★ SIMPLIFIED REMOTE BROADCAST AMPLIFIER
- ★ AUDIO MEASUREMENTS IN AM, FM and TV
- ★ A CHART FOR RESONANT-CIRCUIT CALCULATIONS

1949

NEW Multi-Channel Radio Transmitter with **INDIVIDUAL OVERLOAD PROTECTION**

INDIVIDUAL OVERLOAD PROTECTION

Advanced electronic design provides each unit with individual protection against overloading—failure of any one channel because of overload does not affect operation of others.

VERSATILE MULTI-CHANNEL OPERATION

Each channel provides up to 3,000 watts for continuous wave or frequency shift transmission—2,500 watts carrier for


phone operation. Three basic units—power supply, transmitter, and modulator—permit a variety of combinations through simple channel switching.

TESTED FREQUENCY STABILITY

Meets rigid F.C.C. requirements for ground station operation. Frequency stability within plus or minus .002% at temperatures ranging from 0 to 45 degrees C.

Channel
Switching
Individual
Overload
Protection
Frequency
Stability

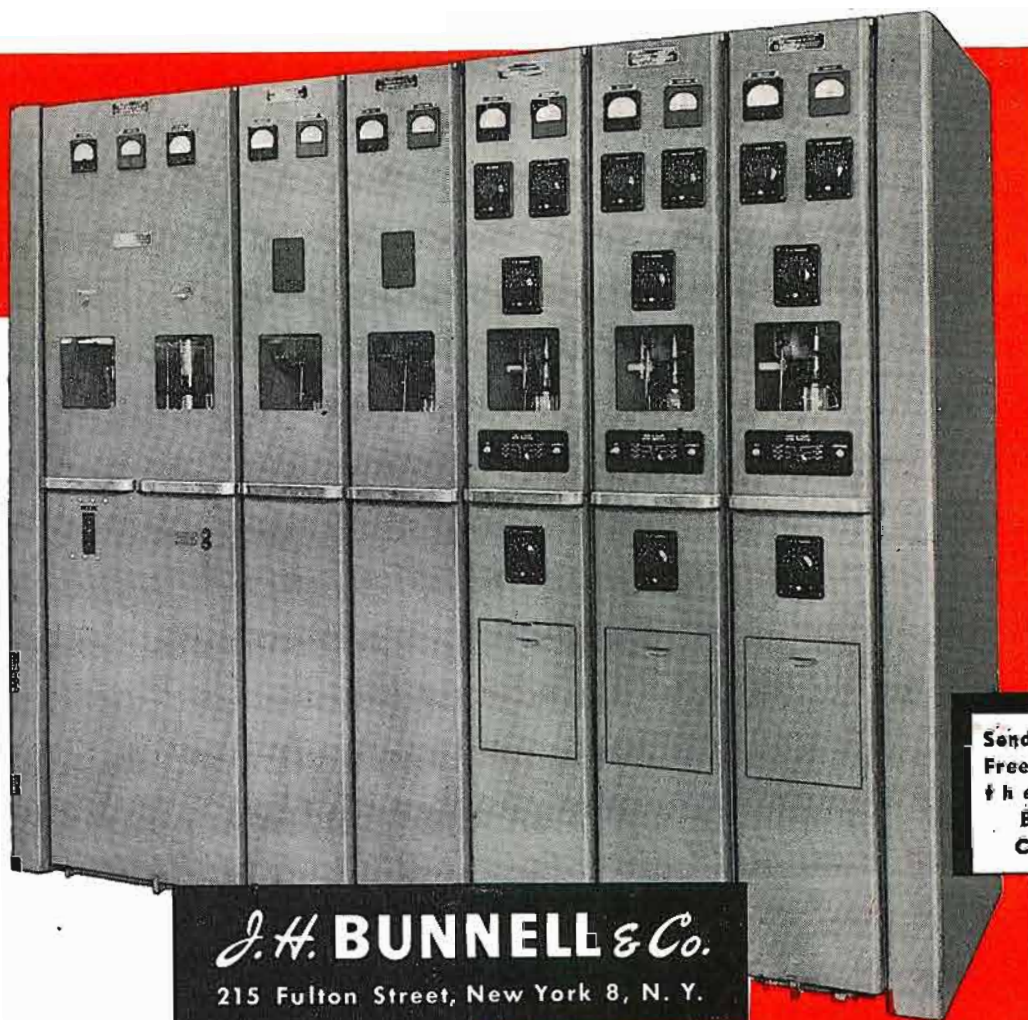Communication
Fidelity
Inverse
Feedback
High Safety
Factors
Primary
Circuit
Switching
Forced Air
Cooling
Low Operating
Cost, Easy
Maintenance



Send for Your
Free Copy of
the NEW
Bunnell
Catalog


J. H. BUNNELL & Co.

215 Fulton Street, New York 8, N. Y.

DEPT. 14

BUNNELL -- A Key Word in Communications Equipment

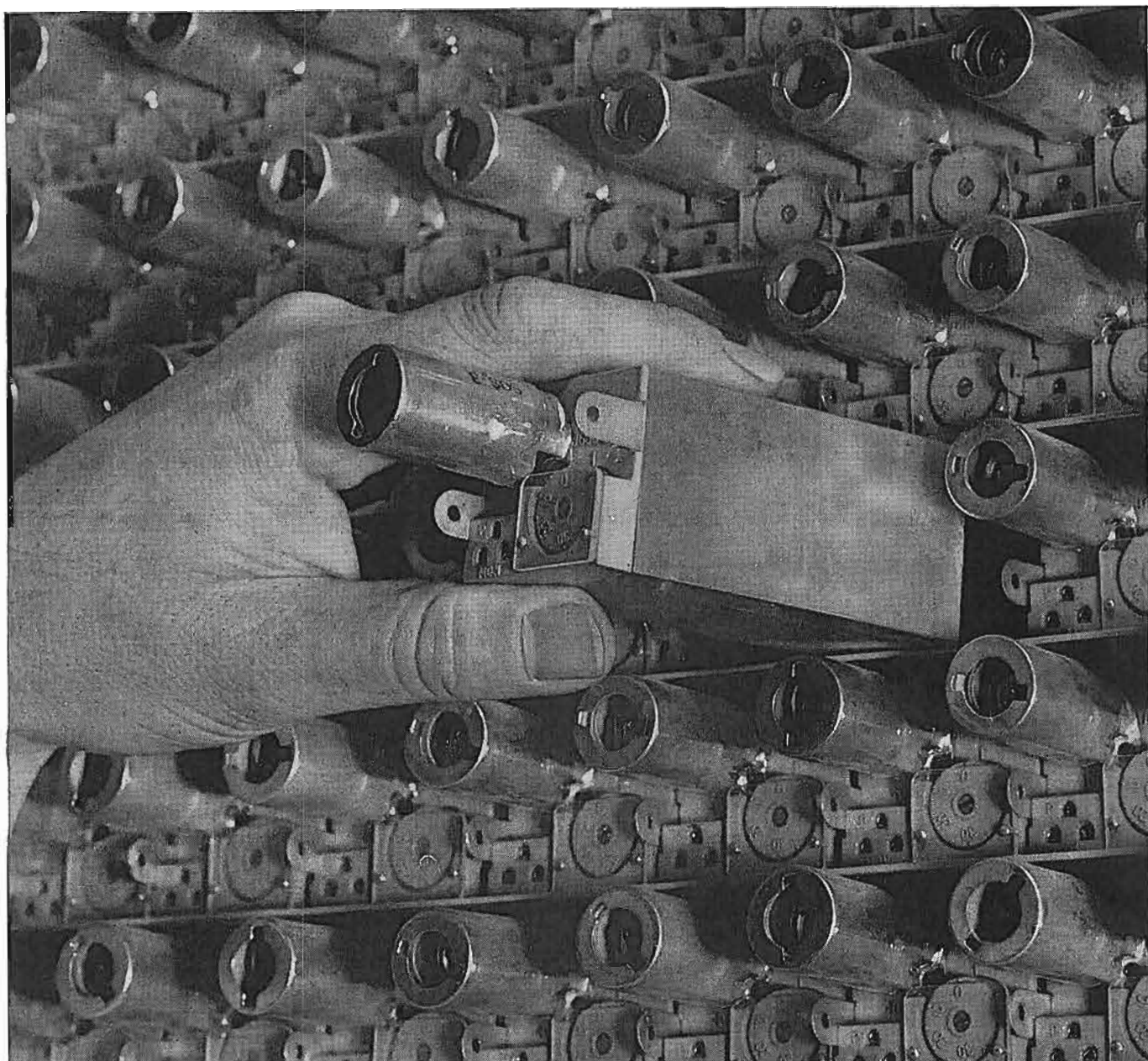Research, Engineering, Production, and Testing facilities for equipment for: Wire Lines • Submarine Cables • Railroad Communication • Radio Airway Systems • Municipal Signaling • Army and Navy Signaling • Carrier Current • Automatic Telegraph • Facsimile



ANOTHER SCORE IN THE

battle of the inches

It takes many costly buildings to house your telephone system. Every inch saved helps keep down the cost of telephone service. So at Bell Telephone Laboratories engineers work constantly to squeeze the *size* out of telephone equipment.

In the picture a new voice frequency amplifier is being slipped into position. Featuring a Western Electric miniature vacuum tube,

tiny permalloy transformers, and special assembly techniques, it is scarcely larger than a single vacuum tube used to be. Yet it is able to boost a voice by 35 decibels. Mounted in a bay only two feet wide and 11½ feet high, 600 of the new amplifiers do work which once required a *room* full of equipment.

This kind of size reduction throughout the System means that

more parts can be housed in a given space. Telephone buildings and other installations keep on giving more service for their size — and keep down costs.

The new amplifiers, which will soon be used by the thousands throughout the Bell System to keep telephone voices up to strength, are but one example of this important phase of Laboratories' work.

BELL TELEPHONE LABORATORIES EXPLORING AND INVENTING, DEVISING
AND PERFECTING, FOR CONTINUED IMPROVEMENTS AND ECONOMIES IN TELEPHONE SERVICE



COMMUNICATIONS

Including Television Engineering, Radio Engineering, Communication & Broadcast Engineering, The Broadcast Engineer, Registered U. S. Patent Office.

LEWIS WINNER

Editor

F. WALEN

Assistant Editor

Bryan S. Davis, President

Paul S. Weil, Vice Pres.-Gen. Mgr.

F. Walen, Secretary

A. Goebel, Circulation Manager

East-Coast Representative:

James G. Mann
2258 Delaware Dr., Cleveland 8, Ohio
Telephone: Erlanger 1728

Pacific Coast Representative:

Brady & Bruce
1002 W. Sixth St., Los Angeles 14, Calif.
Telephone: Michigan 1732
Suite 1234, Ross Building, San Francisco 4, Calif.
Telephone: BUtter 1-2251

Wellington, New Zealand: Te Anu Book Depot,
Melbourne, Australia: McGraw's Agency.

Entered as second-class matter Oct. 1, 1937 at the Post Office at New York, N. Y., under the act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$1.00 per year in foreign countries; 35 cents per copy.

Communications is indexed in the Industrial Arts Index and Engineering Index.

COVER ILLUSTRATION

Morris Barton, chief engineer of KBTU, Dallas, Texas, detailing the operation of a DuMont TV console to Angela Roberts, TV operator-in-training.

CIRCUITRY ENGINEERING

- A Chart for Resonant-Circuit Calculations.....Herbert L. Kraus and Philip F. Ordung 8
Chart Developed for Making Impedance and Admittance Calculations on Tuned Circuits That Are Operating Off Resonance.

BROADCAST MEASUREMENT TECHNIQUES

- Audio Measurements in AM, FM and TV.....Frank H. McIntosh 10
Review of Measurement Equipment and Procedures Required for Gain, Frequency, Harmonic Distortion, Intermodulation, Carrier Shift and Hum and Noise Tests.

COMMUNICATIONS TRANSMITTER DESIGN

- Iron-Core Interstage and Output 3-Kw MF Transmitter Design.....I. F. Deise and L. W. Gregory 12
Part II: Constructional and Operational Features of Transmitter and Transformers.

SOUND ENGINEERING

- Equivalent Circuit Method for Feedback Amplifier Analysis.....T. W. Winternitz 14
Procedure Applicable to Feedback Amplifier Whose Attenuation Frequency Characteristic Is Known, to Determine Its Phase Shift as a Function of Frequency and by Use of Nyquist's Criterion Learn How Much Feedback May Be Used or How Feedback Paths Can Be Altered

BROADCAST STATION INSTALLATION

- That High Power Installation.....Ralph G. Peters 18
What the Transmitting Engineer Faces Prior to and During the Installation of a 50-Kw Job.

AUDIO FACILITIES

- Simplified Remote Amplifier.....William Marsh 22
Equipment Requiring No Operator, Developed for Remotes Where a Single Mike Is Used, Features 6-Watt Amplifier.

MONTHLY FEATURES

- News and Views.....Lewis Winner 7
Veteran Wireless Operators' Association News.....21
The Industry Offers.....28
Last Minute Reports.....32
Advertising Index.....32

Entire Contents Copyright 1949, Bryan Davis Publishing Co., Inc.



Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone MUrray Hill 4-0170



QUICK QUIZ

With a Helpful Answer
FOR COMMUNICATIONS MEN

Problem:

A company has a circuit between offices "A" and "B" consisting of 40 miles of No. 12 BB iron wire. Extending from "B" to "C" is another circuit made up of 25 miles of No. 12 BB iron. Changing traffic conditions call for a direct through circuit from "A" to "C". The use of the existing wire facilities does not provide acceptable transmission since the measured loss is 20 db and requirement is for a 5 db to 6 db circuit. How can this requirement be met?

Possible Solutions:

(a) One possibility would be the replacement of the iron wire with .104 copper wire. This would provide a calculated 4.5 db circuit but present day wire and construction costs would require an expenditure ranging from \$12,000.00 to \$18,000.00.

(b) Another solution would be the use of a voice frequency telephone repeater at location "B" capable of a minimum usable gain of from 14 db to 15 db under all ordinary weather conditions. If such a repeater could be found then this, obviously, would be the correct solution since the cost of a repeater is less than 5% of the cost of wire replacement.

The Logical Solution:

Yes—the logical solution is a voice frequency telephone repeater—if it's a Kellogg Repeater. Here's why—

One of the most important factors in obtaining maximum usable gain in a voice frequency repeater is the limitation of the band of frequencies to be amplified. In the Kellogg repeater this is accomplished in the No. 204 filter which has exceedingly sharp cutoff characteristics outside the voice band, i.e. below 300 cps and above 2700 cps.

Another very important consideration in establishing stable balance at the highest gain is the ability to obtain fine adjustments of resistance and capacity in the balancing net with the maximum of ease. This ideal condi-

tion is provided in the No. 1 balance network of the Kellogg repeater by the use of continuously variable potentiometers (two in each net) and a series of small capacity steps both readily adjustable by hand or screw driver. Thus the time-consuming and comparatively inaccurate method of strapping to adjust for balance is completely eliminated.

Gain adjustments (also screw driver adjusted from the front of the repeater) are accurately calibrated in 1 db steps so that the gain being obtained is always known without the necessity for measurement. Other refinements in Kellogg repeater design include (1) the use of push-pull amplification eliminating harmonic distortion and cross talk or other interference which may be introduced through the power source, (2) the operation of all components at conservative values of current and voltage well below the maximum ratings assuring long, trouble-free life, (3) unit type construction mounting on standard 19" equipment racks thus giving the flexibility necessary for adaption to various circuit requirements, (4) a wide variety of line units for different circuit or signalling functions and (5) provision of test and monitoring jacks for checking tubes and repeater operation.

Kellogg Repeaters are available for operation from either 24 volt or 48 volt battery or from a 105-125 volt 60 cycle AC power source.

Kellogg Switchboard and Supply Company
6650 So. Cicero Avenue
Chicago 38, Illinois

Please send Repeater Booklet to:

NAME _____

ADDRESS _____

CITY _____ STATE _____

SEND FOR OUR REPEATER BOOKLET NOW! ◆

KELLOGG

SWITCHBOARD AND SUPPLY COMPANY

REPEATER

6650 SOUTH CICERO AVENUE • CHICAGO

STAY AHEAD IN CHOOSE

CHARACTERISTICS TYPE 16GP4



Max bulb diameter	16 inches
Max width across diameter	14 1/2 inches
Heater voltage	6.3 v
Heater current	0.6 amp
Focusing method	magnetic
Deflecting method	magnetic
Deflecting angle (approx)	70 degrees
Screen fluorescent color	white
Over-all length	17 1/2 inches (max)
Bulb content	metal-case Fe
Base	standard standard 5 pin

Max ratings, design-center values

Anode voltage	14,000 v
Grid No. 2, voltage	410 v
Grid No. 1, voltage	-125 v

Typical operating conditions

Anode voltage	12,000 v
Grid No. 2, voltage	300 v
Grid No. 1, voltage for cut-off	-55 v

TYPE 16GP4

16-inch metal picture tube, with wide-angle (70-degree) sweep, and high-contrast-glass face. Designed for modern receivers where size of the cabinet is restricted, yet the picture must be large, clear, and sharp. . . . Tube is less than 18 inches long; its weight is approximately half that of an all-glass type. . . . Generous picture area is 163 sq. inches when the entire tube face is scanned; 132.5 sq. inches when standard raster of 3-by-4 aspect is employed. . . . Special high-contrast-glass face helps produce a clear image with superior definition.

Interstage and Output

TRANSMITTER DESIGN

to any combination of *rf* and modulator units up to a total of six.

The plate circuit efficiency of the class *B* power amplifier stage, including output transformer losses, is approximately sixty per cent. The overall transmitter efficiency (that is, useful *rf* power output divided by total power input to the rectifier unit) for the medium frequency transmitter is approximately fifty per cent.

The use of high-frequency iron-core transformers and untuned class *B* circuits have been found to provide many advantages over the conventional tuned class *C* design. The transmitter is only one-third to one-half the physical size of the equivalent class *C* transmitter. The use of class *B* circuits permits voice modulation without a modulator for the power amplifier stage. Since tuning of the transmitter circuits is not required, the operating frequency can be changed with a minimum of moving parts. When class *C* tuned transmitters are operated in parallel for greater power output, it is necessary to compensate for phase changes due to circuit tuning. Since the medium-frequency transmitters use untuned circuits which have a negligible variation in phase shift, they can be operated

Antenna matching transformer employed in the *rf* transmitter. This transformer weighs approximately eleven pounds. The plate voltage of 3500 to 4000 volts for the power amplifier tubes is supplied to the center of the primary winding. The ends of the primary are connected to the tube plates. Spark gaps are provided across each side of the primary to prevent voltage surges from damaging the transformer.



Part II . . . Constructional and Operational Features of Transmitter and Transformers.

by I. F. DEISE and L. W. GREGORY

Westinghouse Electric Corp.

more easily in parallel than the tuned class *C* transmitters.

While the medium frequency *rf* unit described was designed for 2.5-kw output, 5.2 kw power output has been obtained by increasing the drive to the power amplifier stage. This increased grid drive to the power amplifier stage was obtained by increasing the anode potential of the WL-807 second amplifier stage. When thus modified, the medium frequency *rf* unit has a rating of 4.5-kw power output. The medium frequency *rf* unit may be used as a three-frequency transmitter by limiting the types of emission and using an additional crystal oscillator.

Transformer Design


Iron-core transformers designed to operate at medium *rf* are not mate-

rially different in construction or appearance from audio transformers. As in audio transformers, the characteristics of the *rf* transformer are determined by the primary open circuit inductance, the leakage inductance between windings, and the internal distributed capacitance of the transformer. For satisfactory operation the leakage inductance and distributed capacitance of the transformer must be held to low enough values so that the frequency at which the transformer becomes self-resonant is well above the highest operating frequency. These requirements dictate that the size must be as small as possible.

Core loss is an important consideration in *rf* transformers and generally determines the maximum operating flux density.

[To Be Concluded in December.]

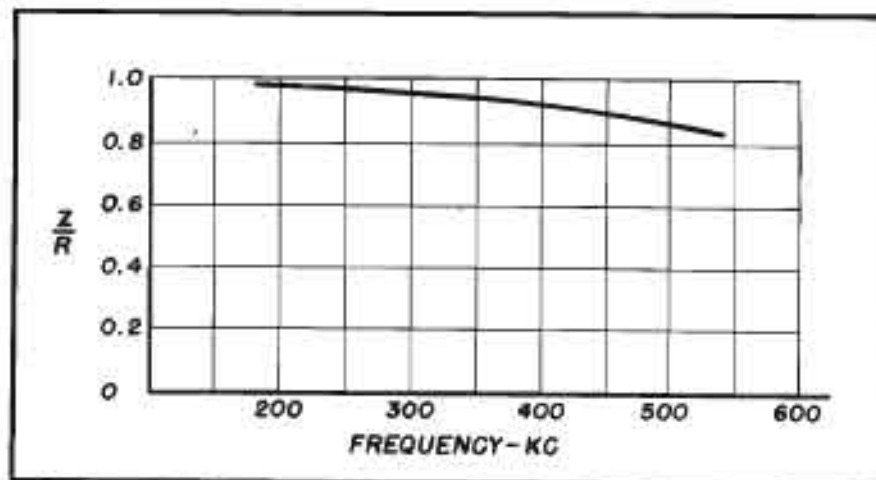Plot of the output transformer variation of impedance with frequency. With this impedance variation the plate current will be approximately 10% higher at 540 kc than at 200 kc for the same output, and thus the efficiency will be slightly lower at the high frequency.



Equivalent Circuit Method For

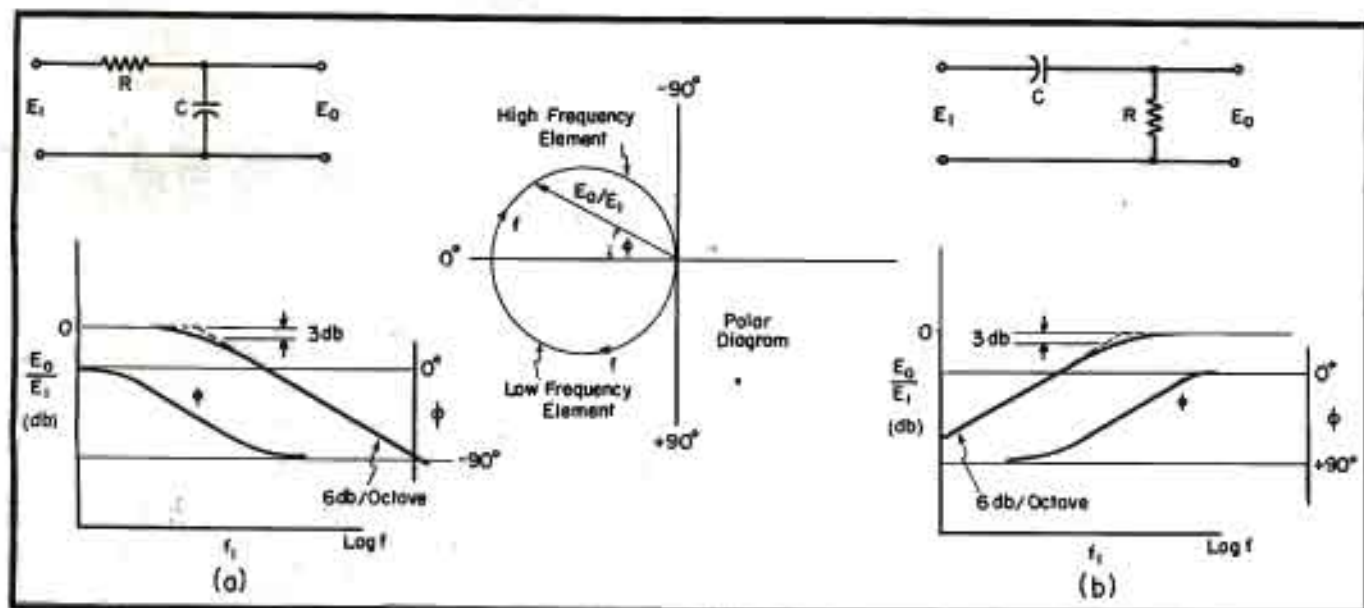


Figure 1
Fundamental elements of the equivalent circuit; (a) the high-frequency element and (b) the low-frequency element.

SUCCESSFUL DESIGN of a feedback amplifier requires careful consideration of the phase shifts of signals over a frequency range considerably larger than the range for which the amplifier will eventually be used; otherwise the amplifier may break into spontaneous oscillation. The circuit may oscillate if any signal, in going through the amplifier and feedback network, suffers a phase shift of 360° or more and has a gain of unity or greater around the loop. The conditions for stability, stated by the Nyquist criterion,¹ are that the locus of the end points of the complex loop gain vector ($A\beta$) must not enclose the point $1 + j0$. In applying Nyquist's criterion it is, therefore, necessary to know both the magnitude and the phase angle of the $A\beta$ vector. Since phase shifts are not easy to measure, the design of amplifiers to which feedback is to be applied also uses Bode's² relation which says that for minimum phase shift networks³ the phase shift depends only on the slope of the attenuation-frequency curve. Using this relation, it is possible to calculate the phase shifts around the $A\beta$ loop, given the attenuation-frequency response of the amplifier and the transmission characteristics of the feedback loop. To apply Nyquist's criterion, these calculated phase shifts can be combined with the measured values of the magnitude of the $A\beta$ vector.

Now, Bode's relation is somewhat difficult to apply in practical cases, but,

as the phase shift of a network depends only on the slope of the attenuation-frequency curve, our problem can be simplified if we analytically substitute a simple network, whose attenuation with frequency is the same or similar to that of the original network, and whose phase shift may be determined by inspection or by simple calculation.

To synthesize any attenuation-frequency curve the simplest possible RC networks can be used as building blocks, and connected to one another by isolating circuits in such a manner that their attenuations in db and phase shifts directly add. The isolating circuits may be thought of as an idealized vacuum-tube amplifier having constant gain, infinite input impedance, and zero output impedance. The fundamental circuits are shown in Figure 1. In (a) appears a simple high-frequency attenuating network and its characteristic curves. The attenuation of this circuit is zero for frequencies somewhat below its cut-off (or break) fre-

quency, $f_1 = \frac{1}{2\pi RC}$, and drops at a

constant rate of 6 db per octave at

frequencies above this frequency. Its response is given by

$$\left| \frac{E_o}{E_i} \right| = \frac{1}{\sqrt{1 + (\omega/\omega_1)^2}}$$

with phase angle

$$\phi = -\tan^{-1} \omega/\omega_1$$

where

$$\omega_1 = \frac{1}{RC}$$

Figure 1b shows a simple low-frequency attenuating circuit which is the same as the high-frequency circuit, but with the positions of R and C interchanged. In this case the gain will drop with decreasing frequency and the phase shift will be positive in sign instead of negative. Its response is given by

$$\left| \frac{E_o}{E_i} \right| = \frac{1}{\sqrt{1 + (\omega_1/\omega)^2}}$$

with single angle

$$\phi = \tan^{-1} \omega_1/\omega$$

To set up an equivalent circuit for a feedback amplifier it is assumed that the attenuation-frequency curve of the $A\beta$ loop is approximately known for all frequencies where the magnitude of $A\beta$ is significant with respect to unity. This may be determined either from a knowledge of the input, output, and interstage networks, or from a few simple gain measurements. Now, using

¹H. Nyquist, *Regeneration Theory*, BSTJ, Jan., 1932.

²H. W. Bode, *Relations Between Attenuation and Phase in Feedback Amplifier Design*, BSTJ, Vol. 19, 1940.

³For a brief discussion of minimum phase shift networks see, for example, F. E. Terman, *Radio Engineers' Handbook*, p. 218.

FEEDBACK AMPLIFIER ANALYSIS

Method May Be Applied to a Feedback Amplifier, Whose Attenuation - Frequency Characteristic is Known to Determine Its Phase Shift as a Function of Frequency, and Thus by Use of Nyquist's Criterion, to Determine How Much Feedback May be Used or How it Must be Changed so that a Given Amount of Feedback Can Be Applied.

by T. W. WINTERNITZ

Cruft Laboratory
Harvard University

as many simple building blocks as necessary, each separately isolated as described, this attenuation characteristic may be closely approximated by sections of straight line attenuations of 6, 12, 18, 24, etc., db per octave.

Equivalent Circuit Problems

In any particular case it may be more or less difficult to set up a suitable equivalent circuit. For the often-encountered case of a resistance-capacity coupled audio amplifier followed by a transformer-coupled power amplifier, it has been pointed out that to realize large amounts of negative feedback it is desirable to make the amplitude responses of the various stages different from one another; so that the attenuation slope will be more gradual.⁴ If this rule is followed, the breaks in the attenuation characteristic will be separated and the various slopes will exhibit themselves directly in the measured data. In any case it should be noted that slopes, which are integrally related to 6 db per octave and therefore may be represented by the equivalent circuit, are the slopes that are normally encountered since they represent changes of amplitude with positive or negative integral powers of frequency.

When the equivalent circuit for the $A\beta$ loop has been constructed, it is a simple matter to calculate the associated phase shift; and, having once found this, one may then investigate the danger points of phase shift, the

frequencies at which the phase shift is 180° either way from the mid-frequency value. If it is found that for the desired amount of feedback, Nyquist's criterion is well satisfied, then, the design will be satisfactory. On the other hand, if it is found that the loop gain is still large for frequencies which have phase shifts approximately $\pm 180^\circ$, it will be necessary to apply less feedback or to alter the design of the $A\beta$ loop to have a slower rate of increase or decrease of amplification with frequency and to re-investigate the new design with a new equivalent circuit.

Example

To illustrate the use of this method, let us suppose that we have an amplifier with a constant gain A_m in its mid-frequency region. We find that its amplification drops off in the high-frequency region approximately as follows:

- At 6 db per octave for one decade above the frequency f' , i.e., in the region $f' \leq f \leq f''$.
- At 12 db per octave for two decades above this, $f'' \leq f \leq f'''$.
- At 18 db per octave from f''' on.

In the low-frequency region the rise of amplification with frequency is

somewhat more gradual than the drop off at high frequencies. It is desired to apply as much resistive voltage feedback to this amplifier as is possible without encountering oscillation. First, we notice that since the attenuation at high frequencies is more abrupt than that at low frequencies, and therefore will be associated with a more rapid phase shift, the high frequencies will control. In other words, it will *sing* at a high frequency if excessive feedback is employed instead of *motor-boating* at some low frequency. Since this is the case, we need only investigate the phase shift at the high frequencies. If the attenuation slope were not more gradual in the low-frequency region than at high frequencies, it would be necessary to investigate the phase shift in the low-frequency region as well.

$A\beta$ Loop Equivalent Circuit

The equivalent circuit for the $A\beta$ loop is shown in Figure 2. It will be noticed that we are neglecting all phase inversions in the amplifier. It is understood that for negative resistive feedback there must be one uncanceled phase inversion in the amplifier, if the feedback is applied from output of the amplifier to input. Thus $A_m\beta$ is inherently a real negative number. Let

$$\omega' = \frac{1}{R_1 C_1}, \omega'' = \frac{1}{R_2 C_2} = 10 \omega',$$

$$\omega''' = \frac{1}{R_3 C_3} = 1000 \omega'.$$

Then for the equivalent circuit

$$\left| \frac{E_o}{E_i} \right| = \left| A\beta \right| = \frac{A_m \beta}{\sqrt{1 + (\omega/\omega')^2} \sqrt{1 + (\omega/10\omega')^2} \sqrt{1 + (\omega/1000\omega')^2}}$$


and the phase angle of $A\beta$, ϕ , is given by

$$\phi = -\tan^{-1} \omega/\omega' - \tan^{-1} \omega/10\omega' - \tan^{-1} \omega/1000\omega'$$


The phase shift is computed in Table 1 (p. 30) and a curve of $A\beta$ and ϕ is given in Figure 3; p. 31. From Figure 3 we see that at the frequency (f_o) the phase has been shifted -180° from its mid-frequency value. Also at this frequency $|A\beta|$ is about 40 db below its value at mid-frequency. This means that the maximum value $A_m\beta$ may have at mid-frequency is 40 db or that the

(Continued on page 30)

Figure 2
Equivalent circuit for the $A\beta$ network of the amplifier discussed as example.

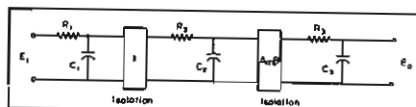

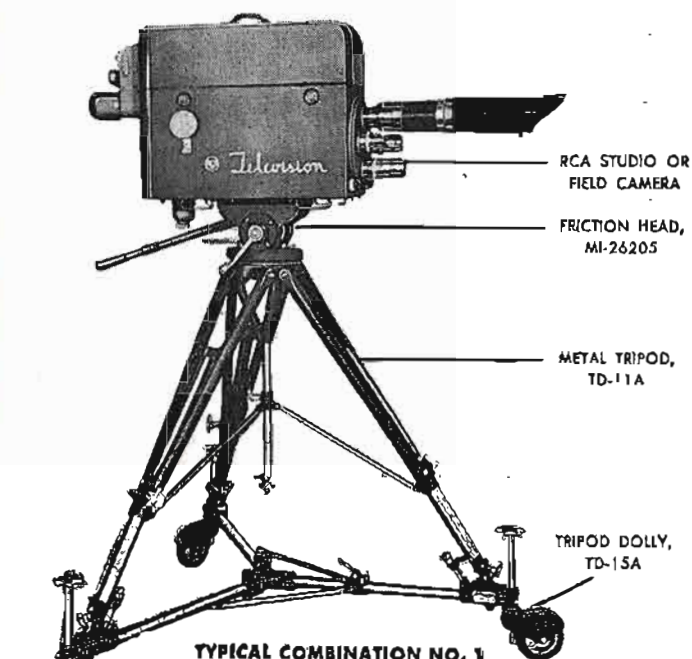⁴For example, see F. E. Terman, *Radio Engineers' Handbook*; pp. 397-8.



TYPICAL COMBINATION NO. 1

Complete camera set-up for maximum operating convenience. *Friction Head, MI-26205* gives camera 360-degree panning and full tilting action. Has "degree-indicator" scales and locking handles. *All-Metal Tripod, TD-11A* uses individual tie rods and center post for sturdy

bracing. Each leg has position calibration and locks. Movable spike points permit set-ups on rough surfaces. Unit folds into compact, self-locking package. *Tripod Dolly, TD-15A* takes up a circular area only 57" diameter. Wheel stops for fixed positions. Folds and carries in a compact package.




TYPICAL COMBINATION NO. 2

A complete vhf relay transmitter for difficult terrain and long distances, where radio relay is more practical than coaxial cable. *Tripod Mount Accessory Kit, MI-26518* provides means for mounting relay equipment to tripod. Includes mounting plate, saddle, and bolts.

Relay Tilt Head MI-26206 provides wide adjustment angles for vertical tilt and horizontal rotation. Sealed bearings for all-weather service. Accurately calibrated. Individual locking handles. *Metal Tripod TD-11A* same as Combination No. 1.

Dollies, booms, stands,

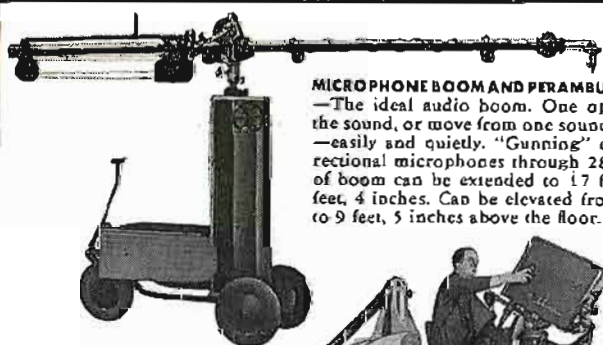


MICROPHONE BOOM AND PERAMBULATOR, MI-26374

—The ideal audio boom. One operator can follow the sound, or move from one sound source to another easily and quietly. "Gunning" device revolves directional microphones through 280 degrees. Radius of boom can be extended to 17 feet; retracted to 7 feet, 4 inches. Can be elevated from 6 feet, 5 inches to 9 feet, 5 inches above the floor.



DE LUXE TV STUDIO CRANE—

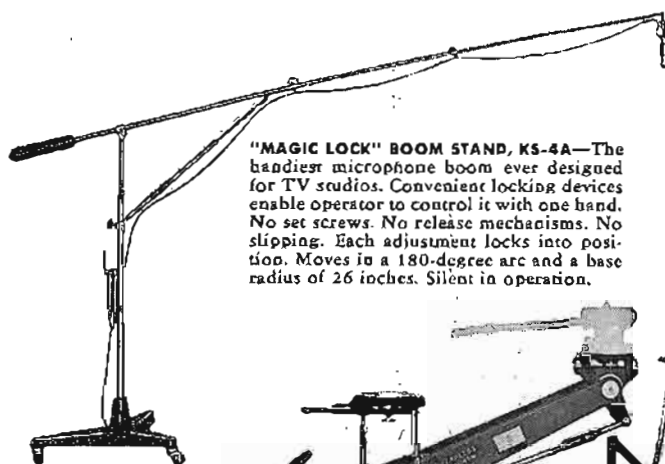
Specifically for large studios. Enables you to get dramatic viewing angles, smooth panning of big scenes, approaches, retreats. Lens height: from 2 to 10 feet above the floor. Full 360 degrees panning around the crane base. 180-degree panning of the turret table. 100-degree up-and-down lift. Turns in a 6-foot radius.




"MAGIC LOCK" BOOM STAND, KS-4A—The handiest microphone boom ever designed for TV studios. Convenient locking devices enable operator to control it with one hand. No set screws. No release mechanisms. No slipping. Each adjustment locks into position. Moves in a 180-degree arc and a base radius of 26 inches. Silent in operation.

STUDIO CAMERA DOLLY, TD-8A—

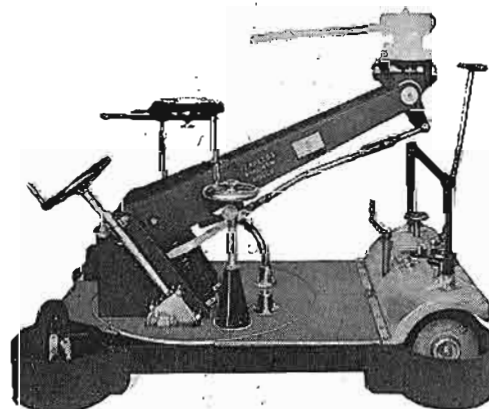Similar to the dollies used in film studios—but both front and rear wheels turn to the side. Entire unit can be moved sideways. Stops lock the dolly in a fixed position. Camera crane boom can be elevated from 23 inches to 74 inches above the floor.



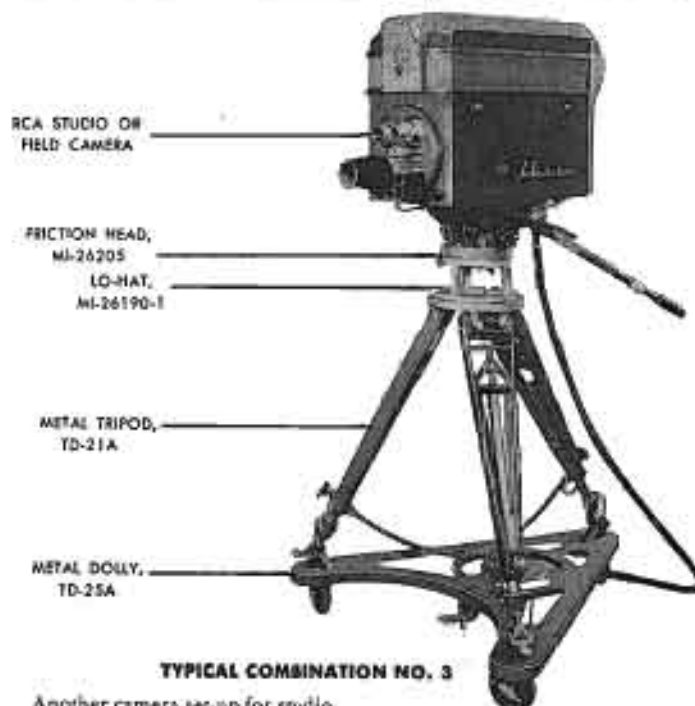

TYPICAL COMBINATION NO. 3

Another camera set-up for studio and mobile work. Handles RCA Studio Camera or Field Camera. Friction Head, MI-26205 same as used in Combination No. 1. Lo-Hat, MI-26190-1 provides greater freedom and height for camera action. Metal Tripod TD-21A for fixed or portable set-ups. Cast

aluminum and stainless steel construction. Legs adjustable up to 21 inches. Dual feet; pointed for field work and flanged for fixed service. Metal Dolly TD-25A. Non-swiveling. Foot-controls for parallel wheel alignment. Individual wheel and tripod locks.



TYPICAL COMBINATION NO. 4

A complete relay pick-up receiving system. Relay receiver and parabola fasten to tripod through Reflector and Parapet Mount, MI-26187. Metal Tripod, TD-21A is set up for rough surfaces.

Field Camera and Friction Head, MI-26205, can be mounted on High Hat MI-26190-2 for wall or parapet use. Complete assembly is attached to Parapet Clamp Support MI-26189.



Here, Reflector and Parapet Mount MI-26187 fasten to Clamp Support, MI-26189—which mounts on top of wall. Relay reflector may also be permanently mounted in wall openings by means of "Gimbal" Antenna Ring Mount, MI-26207 (not illustrated).



mounts, accessories

for every TV set-up



STUDIO CAMERA PEDESTAL, TD-1A—Television's favorite pedestal for studio and other indoor operations. Moves freely, quietly. Crank handle raises and lowers camera to any height between 40 inches and five feet above the floor. Moves in any direction—or about a point. Panning and tilting provided by Friction Head MI-26205.

PICTURED on these pages are typical units and combinations from the most complete line of television accessories in the industry—application-engineered to meet every pick-up situation called for in your TV operations.

This line of mechanical accessories enables you to select just the right combination for your station operation. It includes every device needed for providing universal camera action in the studio and the field. It provides additional flexibility for maneuvering and covering shots from any angle.

RCA TV accessories are stoutly built to withstand the tough wear and tear encountered in field and studio operations. Yet each unit is a model of mechanical simplicity—easy to transport, easy to set up, easy to adjust, and easy to handle.

RCA TV accessories like these are used today in nearly every television station in the country. For complete information on the entire line, call your RCA Broadcast Sales Engineer. Or write Dept. 23K, RCA Engineering Products, Camden, New Jersey.



TELEVISION BROADCAST EQUIPMENT
RADIO CORPORATION of AMERICA
ENGINEERING PRODUCTS DEPARTMENT, CAMDEN, N.J.

In Canada: RCA VICTOR Company Limited, Montreal



That High-Power INSTALLATION

by RALPH G. PETERS

THROUGH CAREFUL search one might discover a broadcast engineer who has never dreamed, secretly or audibly, of installing a high-powered transmitter, particularly the 50-kw AM or equivalent FM or TV setups. You won't find many. Statistics from such a search would reveal that the intensity of the longing is in inverse proportion to the power of the stations said engineer has operated or installed.

With some of the wounds from such a battle still tender allow me to pour a little sober realism over those dream clouds and if the longing persists, more power to you.

In this day and age the construction of any building, large or small, commercial or dream house, involves headaches common to the building trades and material supplies and will not be discussed at this time. The installation of acres of ground system, erection of towers, building of tuning houses, transmission lines and other details incident to getting the fifty thousand or so radiated into the ether are also another story.

Looking backward, the note book reveals that there were months spent in planning and sketching, trying to anticipate everything that would ease the task of installing the transmitter in the new building. The big roll of blueprints supplied by the transmitter manufacturer had to be studied and studied to become familiar with every item, to know just how everything would fit in place. After much prodding from the boss, the building finally reached a state where the transmitter installation could begin, so the transmitter maker was wired to ship at once.

A week or so later a mild sort of shock struck. Seems as if the figures on the blueprint didn't add up to two freight car loads, amounting to some thirty-odd tons of transmitter that were on the siding awaiting our pleas-

ure, with a note to please hurry as the cars and the space were needed. And where was the siding? In the tall weeds a few miles from the transmitter site. This is true because radio stations have to be built in the most inaccessible spots available, and fifty kilowatts appear to go the limit in this respect.

Well, there was nothing to do but make the best deal possible with the machinery mover and get busy, but fast. The precious equipment couldn't be left to the mercies of the weather. The boss had warned that he paid for it. Then the fun began, the piling of all the boxes and crates inside, trying to ignore the pointed remarks of the craftsmen who anticipate moving them around as they complete their work on the building. At the same time an effort was made to try and identify the contents of each of the one hundred and fifty-odd boxes and crates so some attempt could be made at opening them in the proper order. The boys found that this process was aided somewhat by so-called packing lists, with their rows of six-digit numbers bearing a tantalizing relationship to some numbers on the blueprints, but differing enough to pique anyone's sporting blood.

The preliminary data from our equipment friend had assured us that all units would pass through an opening eight feet high, so no extra margin had been allowed in the building design. There was no mention that it would be necessary to remove the crating, a few projecting parts and the supporting beams to be within this limit. Shifting two or three tons of cabinet or transformer on rollers of course is no hardship; dragging it on cement when there is no room for rollers is something else. It offers one an opportunity to exercise your ingenuity and is good training for what is to come.

And then it was found that at least

three of the larger units would have to be hoisted two feet or more to set them over the air pipes already in place.

As assembly began, more intriguing problems arose. For instance, as the final amplifier was being arranged, 'twas found that the three hundred-pound gas-filled capacitors had to hang from the top. Why couldn't they sit on a base, we wondered? And we also wondered why the pressure gauges on these capacitors were placed so that only a midget could squeeze in far enough to read them. Some revolutionary design might have remedied these minor inconveniences, but such a move had no doubt been set aside for inclusion in next year's model.

As the modulator unit was being put together we found our ingenuity taxed again by the problem of making neat right-angle bends in stiff two-inch automobile radiator hose which was to carry cooling air to the top of the big tubes. The instructions stated that the pipe was to go to another pipe. Getting it there was our problem. We were installation engineers now, and such details were to be taken in stride.

In both the *rf* exciter and the final amplifier some inductances and capacitors were romantically identified as *frequency determining parts*. Yes, we too thought the frequency was determined by a crystal oscillator, but don't expect an explanation from your rep; he was just as confused as we were. Somewhere, in early stages of design, an engineer wrote *frequency determining parts*, when he meant *parts determined by frequency*. It became a part of design, and some higher power will have to be called upon to correct it. The problem at hand was to determine whether our friends sent the correct *frequency determining parts* for our frequency (you will find eventually

(Continued on page 24)

New Higher Power Electron Tube with All-Ring Seals

Now Available for Full Power
Operation Up to 110 mcs/sec.

The availability of the Machlett ML-354, a compact, super-power water and forced-air cooled triode for operation up to 110 mcs/sec. in FM, AM, TV and industrial service is a contribution of significant proportion to progress in all fields of electronic development. The tube is provided with coaxial filament, grid, and plate seals, making it ideally suited to cavity-type circuits.

Superior Design Features

Developed to satisfy the need for higher-power electron tubes in broadcast, communications, research, and industrial services, this all-ring-seal triode is of a balanced electrical and mechanical design. Its low plate impedance makes it ideally suitable for broad band applications. All electrodes mount directly from heavy copper cylinders, resulting in a structure which is far superior, electrically and mechanically, to conventional water-cooled electron tube design; all glass-to-metal seals are of Kovar, and the large diameter seals give increased strength and freedom from excessive heating at electrode contacts. The tube incorporates a high-conductivity, heavy-wall copper anode. The integral anode water jacket and quick change water-coupling, contribute to easy and rapid tube replacement. The cathode is a 16 strand self-supporting thoriated-tungsten filament, completely balanced and stress-free throughout life. The rigidly supported grid and cathode are designed to give uniform anode heating. The grid is capable of unusually high heat dissipation contributing to maximum stability of tube performance and circuit operation.

Wide Application

The foregoing design features and characteristics are incorporated in the ML-354 triode, developed by Machlett Laboratories, Inc., Springdale, Conn. The ML-354, having basic design features usable over a wider range of power and frequencies than has been heretofore available in triodes, finds applications, among others, in high-power AM, FM and TV broadcasting, cyclotron and synchrotron oscillators and in induction and dielectric heating.



DESCRIPTION

The ML-354 is a compact, general purpose, high power electron tube designed for operation at full power up to 110 mcs/sec. It is an all-ring-seal water and forced-air-cooled triode capable of giving in excess of 50 kilowatts output power at 108 mcs/sec. in grounded grid circuits with 10 kilowatts driving power. Considerably higher power is available at lower frequencies. This tube is ideally suited for cavity operation, and its low plate impedance is advantageous for broad band applications. Features include Kovar glass-to-metal seals, sturdy electrode structures, integral anode water jacket, and quick change water coupling. The cathode is a stress-free self-supporting thoriated-tungsten filament.

GENERAL CHARACTERISTICS

Electrical

Filament Voltage	12.5 volts
Filament Current	220 amps
Amplification Factor	25
Interelectrode Capacitances	
Grid-Plate	65 uuf
Grid-Filament	83 uuf
Plate-Filament	2.4 uuf

Mechanical

Mounting	Vertical, Anode Down
Water-flow on Anode	
for 75 KW Dissipation	45 gpm
for 50 KW Dissipation	30 gpm
Air Flow on Seals	
to limit glass to 165°C.	220 cfm
Net Weight, approximate	40 lbs

MAXIMUM RATINGS: Radio-Frequency CW Oscillator

	Max. Freq. 50 mcs/sec.	Max. Freq. 110 mcs/sec.	
DC Plate Voltage	15	9	kVdc
DC Plate Current	13	13	Ade
DC Grid Voltage	-1.6	-1.6	kVdc
DC Grid Current	2.5	2.5	Ade
Plate Input	195	100	kW
Plate Dissipation	75	50	kW

For complete technical data on the ML-354 high power, all-ring-seal triode, write to Engineering Department,

MACHLETT LABORATORIES, INC.

Springdale, Conn.



OVER 30 YEARS OF ELECTRON TUBE EXPERIENCE





FIELD TESTED

Installation Information on

TV and FM

RECEIVING ANTENNAS

TV...FM Antenna Installation

by IRA KAMEN,

Manager, Antenaplex and TV Dept., Commercial Radio Sound Corp.

and LEWIS WINNER,

Editorial Director, Bryan Davis Pub. Co., Inc.; Editor, SERVICE and COMMUNICATIONS

The only practical book on the all-important item in TV and FM reception . . . based entirely on actual experiences in the most active TV and FM areas in the country. . . . Over 35,000 words of vital data with over 130 photos and drawings.

TEN CHAPTERS COVERING:

Installation Tools
Antenna Installation Procedures
Securing 12-Channel Coverage
HF Antenna Installations
TV Interference

Fringe Reception
Master Antenna Systems
FM Antennas
Installation Business Practices
Tricks of the Trade

The first book in which you'll find complete design and installation information on every type of TV and FM receiving antenna. . . . Contains detailed illustration and subject index for rapid reference.

✓✓ "The best book on the market at this time dealing with the problem of television antennas and antenna installation . . . If more Service Men would read this book, it would help them considerably in making better installations and providing better television reception for their customers."—M. J. Shopp, President, Jerrard Electronics Corp.

✓✓ "Will recommend it to all the Service Men and technical people I meet."—Charles Coko, Field Service Engineer, Bendix Radio.

✓✓ "Well organized and illustrated, very complete and up-to-date, carefully detailed. It will definitely improve the ability of the man who studies it and therefore is mighty useful to a firm like ours."—Hamilton Hoge, President, United States Television Mfg. Corp.

✓✓ "Will certainly fill a long-felt need for some practical information . . . sincere congratulations."—George P. Adair, Former Chief Engineer, FCC, and now Consultant in Washington, D. C.

✓✓ "A thorough-going compendium of the installing art . . . Going to recommend it highly to our Service Control Department and our service organizations."—Ernest A. Marx, General Manager, Television Receiver Sales Div., Allen R. DuMont Laboratories, Inc.

✓✓ "Informative and extremely well written."—R. Morris Pierce, Vice President in charge of Engineering, WJR, WGAR, KMPC.

BRYAN DAVIS PUBLISHING CO., INC., Book Dept.
52 Vanderbilt Avenue, New York 17, N. Y.

Send me a copy of TV . . . FM Antenna Installation, post-paid, for which I am enclosing \$2.00.
(Please print)

NAME

ADDRESS

CITY AND STATE

AT YOUR JOBBER
OR ORDER DIRECT



Price \$2 Post Paid



Fall Meeting

THE ANNUAL Fall meeting at the Fire-place Inn, New York City, attracted quite an audience, with many old-timers and out-of-towners appearing for the first time in years. Up from New Orleans was Paul Jensen; from St. Louis, George Martin, and from Cleveland, G. P. Shandy. VWOA vice president Haraden Pratt, who had been ill for many months, came down, too.

Others at the get-together included Henry Hayden, VWOA assistant secretary and his guest S. B. Allen; Paul Trautwein, who hasn't been around for a long while; Joe L. Savick; Roscoe Kent; A. J. Stobbart, who came down from Philadelphia; Stan Wolff, from Brewster, N. Y.; Joe T. Maresca; Jerry Goldrup; R. H. Pheysey, Tony Brizzolari; Frank Orth; George Duvall; Sam Schneider; Charles R. Shanholtzer; R. K. Davis; H. B. Koch; Pete Podell; Benny Beckerman; Ken Richardson; H. H. Parker; E. N. Pickerill; C. D. Guthrie; Arthur Costigan; Geo. Clark; Bill McGonigle, ye prexy; Bill Simon, ye secretary; H. T. Williams; Joe Maloney; Arthur Rehbein; John Lohman; Gene Cochran; J. P. Laurant; Robt. L. Fischer; Tony Tamburino; Vic Villandre; Dave Little; G. I. Martin; G. P. Shandy and Marvin Seimes. . . Lt. Comdr. D. A. Bark advised he couldn't attend since he was in Astoria, Oregon, at the U. S. Naval Station. . . Jim Marcroft reported that he was busy at Hicksville, L. I., with Press Wireless. . . Milton King notified the committee that he was leaving for a vacation, and would thus be absent. . . George Bonadio said he was just too busy. . . Monte Cohen, E. H. Price, A. Barbalate, Don McNicol and Wylie Paul wrote in for reservations, but were prevented from attending because of QRM. . . L. H. Marshall was on his way to the Azores aboard the USNT Peconic and thus couldn't come to the affair. . . Pat O'Keefe was bound for banana land aboard the SS Jamaica that night and so was S. G. Scruggs on the SS Junior. . . R. S. Henery was busy out at Rocky Point. . . Due to illness L. C. Nunn could not be present. . . F. C. W. Lazenby was away on a lecture tour out west. . .



At a recent VWOA dinner meeting in New York City, front to rear: Ray Morehouse, R. J. Iversen and C. D. Guthrie.

Max F. Ortely could not make it because of duty. . . Harry Cornell was on vacation. . . Jack Poppele sent in a reservation, but developed a bad cold. . . Roger Lum was out of town.

Personals

YE PREXY announced at the Fall meeting that the VWOA Dinner-Cruise in February, 1950, celebrating our 25th anniversary, will be an outstanding event. . . VWOA life member Raymond Guy has been elected president of the IRE for 1950. Congratulations. . . Geo. Clark has reported that the Monument Committee will soon present plans to the N. Y. City Hall boys concerning the relocation of the Radio Operators Monument. . . Tom Gardner advised that he was changing his address from Portland, Oregon, to Galveston, Texas, to become Radiomarine service manager in that port. . . Charles M. Hodge has written in from Dhahran, Saudi Arabia, where he is employed by the Arabian American Oil Co. . . Al Koehler wrote in to say that he enjoys hearing via COMMUNICATIONS about some of his old friends. . . G. G. Benson must be quite busy down in Jackson, Mass., for it's been many months since he's con-

tacted us. . . Glad to see that dues funds are coming in early this year. Thus far we've heard from H. K. Bergman, who is with WGY, Schenectady; H. B. Black, Monte Cohen, who is treasurer and executive vice president of F. W. Sickles, Chicopee, Mass., and H. L. Cornell, who is with Socony Vacuum, and has been extremely busy during the last few months completing the company's radar installation program. . . H. D. Kaulback, Commander, USN, is now stationed at First Naval District headquarters, serving as District Reserve Electronic Warfare Program Officer. . . William S. Marks, commenting on his early days in radio, reveals that he began back in '17 while he was in the Navy. He attended Harvard University Naval Radio School at that time, and in '19 he obtained his First Class Commercial Radio license and started his commercial career aboard the SS Warwick. Also sailed aboard the SS Birmingham City, SS Dannedauke, the old Shipping Board vessels. Later he sailed on the Vacarro out of New Orleans, and Black Diamond and Isthmian out of New York City. He is now chief engineer of the Coles Signal Laboratory, Fort Monmouth, N. J., where he has been located since '30, except for an active duty period in the Signal Corps from '42 to '46 as Lt. Colonel. . . Old-timer H. D. Taylor was recently honored on his 25th anniversary with WITC in Hartford, Conn. He started there back in '24 as chief operator. For the last eight years he has been plant engineer and chief engineer. . . Don De Neuf, who for the last two years has been chief engineer of the Rural Radio Network, is now assistant general manager in charge of engineering and station relations. . . VWOA life member Brigadier General David Sarnoff, chairman of the board of RCA, received the Peter Cooper medal for the Advancement of Science and art at the recent convocation ceremonies in N. Y. City honoring Cooper Union's 90th anniversary. DS was selected by a jury of nine presidents and deans of engineering schools and colleges in the New York area, for outstanding service in the advancement of science in its practical application to life.



Left, front view of remote broadcast amplifier. The small unmarked bakelite plate, at the lower left side of the panel, hides the output transformer taps. Removal of this cover allows attachment of suitable loudspeakers, permitting use of the unit as a low power *pa* system. To act the volume, while the amplifier is operating at low gain, a double 3,500-ohm potentiometer front-panel control is used. It was found necessary to use a panel-operated control, in this case, not only to compensate for necessary variations in the studio *cue* feed, but because of varying requirements at the pickup point.

Internal view. The amplifier is mounted in a cabinet with a hinged lid which may be raised for access to the tubes. The panel, which is removable, mounts the amplifier.



SIMPLIFIED Remote Amplifier

by WILLIAM MARSH

Chief Engineer
WHHM, Memphis, Tenn.

Simplified equipment has always been found extremely handy, particularly at the small station with limited manpower. This was demonstrated quite effectively a short while ago at our station, when a simplified remote amplifier was developed.

The amplifier, designed for remote broadcasts of a recurring nature, was found ideal for operatorless pickups from churches, man on the street, night clubs, or any other occasion where a

Equipment, Requiring No Special Operator, and Developed for Remotes where Single Mike is Used, Features 6-Watt Amplifier With Provision for Switching Terminations, Gain and Function.

single microphone pickup could be used.


The basic amplifier used was a six-watt unit¹ with low impedance output

from one 6L6. The amplifier was mounted in a cabinet,² which has a hinged lid which may be raised for access to tubes. A carrying handle is bolted to this lid. A speaker was mounted in one louvered end of the cabinet.

The remote setup is essentially an amplifier with means for switching terminations, gain, and function. When used for receiving a *cue*, it is a low gain line-bridging amplifier which operates into a loudspeaker, and when used for originating a broadcast, it is a high gain microphone amplifier which feeds a line.

Gain is regulated in the remote amplifier by means of two volume controls. One control, which sets the

(Continued on page 26)

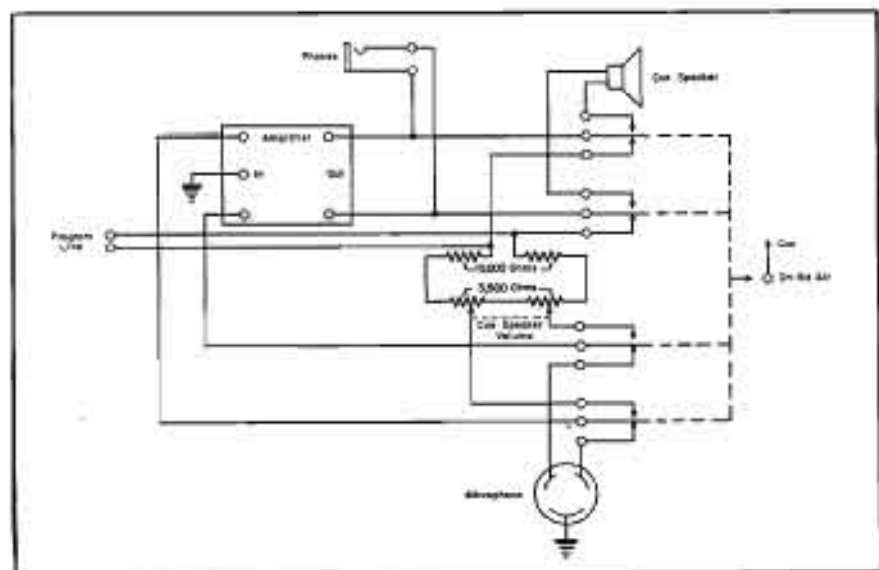

¹ECA M1-12218, *Bud C1747.

²Circuit of the amplifier which requires no continuous operator for control.

Designed for Application



90651

The No. 90651 GRID DIP METER

The No. 90651 MILLER GRID DIP METER is compact and completely self contained. The AC power supply is of the "transformer" type. The drum dial has seven calibrated uniform length scales from 1.5 MC to 270 MC with generous over laps plus an arbitrary scale for use with special application inductors. Internal terminal strip permits battery operation for antenna measurement.

**JAMES MILLEN
MFG. CO., INC.**

MAIN OFFICE AND FACTORY
**MALDEN
MASSACHUSETTS**



High-Power Installation

(Continued from page 18)

that they did), and how they fit into place. A good deal of head-scratching, a lot of cigarettes and possibly a few naughty words later we found, by counting turns, consulting tables, and trying various wrong combinations that there was a way to get most of them in position. One or two wouldn't fit, or didn't appear to have any discernible use, but that was a problem for tune-up time, so why worry now?

When wiring between units began more interesting problems developed. Apparently many of the vital and complex control centers had been built for our transmitter supplier by *Private Electric*. Now *P. E.* were no amateurs at this construction business, but someone didn't spend much time coordinating what the transmitter boys wanted, or thought they wanted, with what *P. E.* thought they should have. Claiming a few ideas of their own, *P. E.* found a number of innovations and refinements worthy of inclusion in the design and proceeded to use them. After building a few, more changes were suggested, and these were added in later units. In a few cases the transmitter producer thought enough of the improvements to recognize them and modify their blueprints to suit. In others, they were ignored, overlooked, or forgotten so no one but *P. E.* ever appreciated the changes.

Our set of blueprints showed some late changes which were not incorporated in the unit that came with our transmitter. In a job sent to one of our neighbors his model was too early to have corrections included. These changes caused quite a bit of grief when the current was applied.

A two-hundred-forty-volt relay connected so that the voltage was across only half the winding functioned apparently as it should, for a time. Then someone noticed the smoke and the smell and after hurriedly opening switches the hunt was on. When the hot spot was located a long distance call was initiated for a new coil. While waiting for it to cool enough for handling, three yards of blueprint had to be studied to see how its operation could be bypassed for the present so tests could continue.

We found a fan for cooling this control center, but nothing resembling a mounting bracket nor any hint as to where it should be mounted. We took a little justifiable pride in our very own solution, only to be told that, in the first place, the fan wasn't really necessary anyway, and in the second place, that a more effective cooling job

could be done by providing an extension from the large transmitter-cooling duct under the floor. We immediately saw the wisdom in this advice but wondered why it wasn't pointed out before the cement floor was poured. Putting another pipe through a six-inch cement floor with the aid of chisels and star-drills wasn't our idea of light work.

One of the sales features of our transmitter was the almost human system of overload protection and indication. There was a colored lamp or a little red flag to show almost everything that could happen except a wow in the disc-jockey's favorite record. The machinery to operate this electrical brain was necessarily complex, and we were a little tolerant of our supplier's failure to completely understand just what *P. E.* built into it. Our luck was good and we were able to secure the services of a local *P. E.* expert to check the adjustments and repair minor defects. If you're not that lucky your session with the cams, pawls, resets, over-voltage cut-offs, under-volt-

STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACTS OF CONGRESS OF AUGUST 24, 1912, AND MARCH 3, 1933, OF COMMUNICATIONS.

Published monthly at New York, N. Y., for October 1, 1949.

State of New York) ss:
County of New York)

Before me, a notary, in and for the State and county aforesaid, personally appeared B. S. Davis, who, having been duly sworn according to law, deposes and says that he is the Business Manager of COMMUNICATIONS, and that the following is, to the best of his knowledge and belief, a true statement of the ownership, management, etc., of the aforesaid publication for the date shown in the above caption, required by the Act of August 24, 1912, as amended by the Act of August 1933, embodied in section 337, Postal Laws and Regulations, to wit: 1. That the names and addresses of the publisher, editor, managing editor, and business manager are: Publisher, Bryan Davis Publishing Co., Inc., 52 Vanderbilt Avenue, New York 17, N. Y.; Editor, Lewis Winner, New York, N. Y.; Managing Editor, None; Business Manager, B. S. Davis, Ghent, N. Y.; 2. That the owners are: Bryan Davis Publishing Co., Inc., 52 Vanderbilt Avenue, New York 17, N. Y.; B. S. Davis, Ghent, N. Y.; J. C. Munn, Union City, Pa.; A. B. Goodenough, Port Chester, N. Y.; P. S. Well, Great Neck, N. Y.; F. Walen, Tuxedo, N. J.; G. Well, Great Neck, N. Y.; L. Winner, New York, N. Y.; 3. That the known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities are: None. 4. That the two paragraphs next above, giving the names of the owners, stockholders and security holders, if any, contain not only the list of stockholders and security holders as they appear upon the books of the company, but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting is given; also that the said two paragraphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock, and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association, or corporation has any interest direct or indirect in the said stock, bonds, or other securities than as so stated by him.

(Signed) B. S. DAVIS, Business Manager.

Sworn to and subscribed before me, this 14th day of September, 1949.

(Seal) NATHAN JELLING,
Notary Public.

Commission expires March, 1950.

age releases, interlocks and regulators will be educational to say the least.

A part of this protection system usually comes packed under the title of *protective relay*. Our blueprints showed the necessary wiring for it, but was quite non-committal about where it is supposed to mount. We found that our supplier didn't know either. We had to brush up our ingenuity again and find a place to get it out of the way and still run wires to it.

The interesting purpose of this *protective relay* is to turn on a red lamp to show when the carrier is on, and another lamp to show when it is off. We found that there was a slight duplication of functions here, since several meters and lamps had been placed on the transmitter to remind us when the power was on, with the aforementioned system of overload relays taking care of any unorthodox power application. If you've soaked up enough *rf* theory to get your license, and acquired enough broadcast experience to warrant a fifty-kilowatt job you have a fair chance of being able to tell without an indicator lamp whether your carrier is on or off. But it is a refinement, and the colored lamps help impress the *boss*.

Another *modern design* feature in our job was the use of pairs of red and black push buttons instead of tuning knobs or indicating dials. It was decided that broadcast engineers would live longer, and possibly work for lower wages if not required to strain their muscles turning knobs. With the negligible complication of a tuning motor, insulated shaft, universal joints, push-buttons and the associated wiring, this back-breaking task was said to be eliminated. Tuning we were told is now as simple as pushing a button. Since it was not considered essential to provide a front panel indicator, the appropriate meter had to be watched to see what happens. If the reading changes in the manner expected, well and good. If it went the wrong way the other button was to be pushed. It's as simple as that, we were informed. If it doesn't change at all, well either the variable inductance or capacitor was at the end of its travel against the stop, or it was stuck and the motor stalled, or one of the couplings was loose and the shaft had begun to slip or the wrong meter was being looked at. The last possibility, that something was amiss in the circuit, was found to involve *rf* theory. This our friendly supplier took great pains to avoid.

When the moment arrives for turning on the full *fifty-thousand watts* into either a radiating system or a

(Continued on page 26)

you get these **PLUS** values in
VITROHM RESISTORS



check each **PLUS**

PLUS...Ceramic Materials and Cores—of high density, low porosity and high dielectric, with correct thermal co-efficient of expansion—developed and produced by Ward Leonard!

PLUS...Exclusive WL Vitreous Enamel—tough, crazeless, moisture-proof, and acid-proof!

PLUS...Specially Drawn Resistance Wire—and Uniform High Precision Winding!

PLUS...Consistent Accuracy and Stability—even under extremes of temperature, humidity, corrosive atmospheres, shock, vibration, altitude!

PLUS...All Connections *Silver-Soldered*—with special silver solder developed in the WL laboratories!

PLUS...Terminals of special alloy, designed to provide the strongest anchorage!

PLUS...Careful adherence to resistance tolerance!

PLUS...Direct, Complete Control over physical, chemical and electrical qualities—to assure properly matched component characteristics and constant uniformity!

PLUS...Wide Range of Stock Types—as well as Vast Variety of Special Units!

PLUS...Proved Over Half a Century of Resistor Experience in all types of applications!

Electronic Distributor Division

WARD LEONARD ELECTRIC CO.
53-M West Jackson Blvd., Chicago 4, U.S.A.



SEND FOR
STOCK-UNIT
CATALOG D-130
Gives helpful data
on Resistors and Rheostats available from
stock...lists Radio
Amateur Relays.

WARD LEONARD
RESISTORS • RHEOSTATS • RELAYS

WHERE BASIC DESIGNS ARE RESULT ENGINEERED FOR YOU

insuline *has it!*



**PJ-055B . . . The PLUG
MANUFACTURED TO
MEET THE LATEST JAN
SPECIFICATION P-642**

INSULINE Plug PJ-055B is the new precision-made plug manufactured to meet these precise requirements. It's designed for long life and efficient service under any climatic and operating conditions.

**IMMEDIATE DELIVERY!
ANY QUANTITIES!
SPECIAL QUANTITY PRICES!**



Actual size showing interior detail



High compression-molded Resinox insulation gives the PJ-055B extremely high dielectric and tensile strengths. The molded Resinox shell combines extreme durability with high dielectric, low moisture absorption characteristics.

A complete catalog of INSULINE products is available upon request



insuline

CORPORATION OF AMERICA

INSULINE BUILDING • 36-02 35th AVENUE • LONG ISLAND CITY, N. Y.
West Coast Branch and Warehouse: 1335 South Flower Street, Los Angeles, Calif.
QUALITY PRODUCTS SINCE 1921

Coming soon



... watch for announcement!

(Continued from page 25)

dummy load, you may experience as we did some let-down in the thrill anticipated. This is partly due to unimaginative mathematics, which shows a current increase to only about fifteen amperes, considering a 230-ohm line.

Mentally comparing this to the almost five amperes used for five kilowatts or the six and a fraction for ten kilowatts and it is suddenly realized that 50,000 watts is not such terrific power after all.

With a bow toward our supplier (and *Private Electric*) we also conceded the ease with which the increased

power could be handled. The five or six amperes of plate current were found as *matter-of-fact* as the six hundred mils you may have been used to. The large but unspectacular rectifiers provide their ten or twelve amperes of 10,000-volt dc as calmly as 866s.

If you've been conscientious about grounding and shielding you'll find, as we did, there are no shocks from touching metal parts in the building, no lamps burning with the switch off, and no rf in the audio circuits. And operation was found to be as stable as with our belated thousand-watter.

But what a time we had before we found out!

Remote Amplifier

(Continued from page 22)

amplification while the amplifier is operating at high gain, is a screwdriver control instantly available through an opening in the rear of the unit. The installation engineer sets this control so that the amplifier will furnish an average level, correct with respect to the program source. A jack on the front panel allows headset monitoring during setups.

A four-pole double-throw key switch* performs all program switching functions. One pair of poles transfers the amplifier output from the line to the loudspeaker, and another pair transfers the input from the microphone to the line-bridging network and cue volume control.

As telephone lines are frequently used without isolation transformers, it is imperative that no grounded or unbalanced circuit be connected to them. Accordingly in this case it was necessary to remove the ground normally found on one side of the output transformer.

Since appreciable power may be transferred from the amplifier to the speaker, the speaker was carefully matched to the amplifier. The microphone also received this close attention, with its impedance matched into the amplifier. To reduce level without appreciable loading or distortion, an intentional mismatch was included in the bridging connection.

The amplifier-output transformer connection, normally used for the speaker, is connected to the telephone line when the equipment is being used to feed the line. While this is actually a bad mismatch from the amplifier standpoint, it is unimportant because the amplifier has inverse feedback, and is being used well below its rated power output. The line merely sees the amplifier as a generator, with a comfortably low internal impedance and adequate ability to furnish a +8 dbm required, with no apparent distortion. Measured distortion values are on the order of two per cent.

In application at, let us say, a night club for an orchestra pickup scheduled from 11 to 11:30 PM nightly, the line is installed, the orchestra leader shown the remote amplifier by an engineer or production man and a musical setup arranged. Henceforth at about 10:30 PM, each following night, the orchestra leader turns on the amplifier. He then adjusts the cue volume, which amplifies the cue program coming down the program line from the studio, and listens briefly to make sure that

*Scromberg.

the cue program is present. Then he turns the gain down and goes on about his business.

At a few minutes to 11 PM the handman turns up the gain again so that he and the band can hear the cue, and at 11 PM the studio announcer gives the cue, which is heard through the loudspeaker. Then the band leader flips the key switch and he is on the air. At the end of the show, the orchestra leader can push the cue switch down again and hear the studio announcer acknowledging the program if he wishes. The leader then turns the amplifier off, and the remote program is over for one more night.

Incidentally it is rather remarkable how effective a one-mike pickup of a 12-piece orchestra can sound, when the band director realizes that he must make the band fit the microphone.

The unit has provided very dependable service at WHHM, one being used for two nightly broadcasts from a night club for a year and a half, with only four routine service calls required.

Audio Measurements

(Continued from page 11)

should be measured in terms of db below 100% modulation. The standards require that the total noise in the 50 to 15,000-cycle band shall be at least 60 db below the audio-frequency level, representing a frequency swing of ± 75 kc (± 25 kc for TV stations). The noise-measuring equipment should be provided with a standard 75-microsecond deemphasis circuit, the time constant of the meter in the noise measuring circuit being similar to that of a standard vu meter.

Noise Level Measurements (AM): The regulations require that measurements should be made on the amplitude modulated noise at the output of the transmitter. The requirements of the standards are in terms of db below 100% amplitude modulation. Since most modulation monitors for FM stations do not include demodulators for amplitude modulation, this is a difficult measurement to make. Since the RMS of the rectified envelope of a 100% amplitude modulated wave is equal to the RMS of the carrier itself, it can be assumed that a measurement of the ratio of the amplitude modulated noise to the carrier itself will give the desired figure. The problem then is to measure the RMS of the carrier and the RMS of the noise wave form. The ratio of these quantities, expressed in decibels, provides the figure required by the standards; according to the standards this value should be greater than 50 db.



...punching dies available in endless Variety for COSMALITE COIL FORMS

Manufacturers of radio and television receivers KNOW the outstanding advantages of COSMALITE in both performance and price.

There is a further saving in time and costs through the use of our extensive number of dies available to purchasers of Cosmalite Coil Forms. Punched, threaded, notched and grooved to meet your individual specifications.

*Reg. U. S. Pat. Off.

Tell us your needs. Quite probably we can be of value to you in your planning and production. Your inquiry will receive personal and experienced attention.

The CLEVELAND CONTAINER Co.
6201 BARBERTON AVE. CLEVELAND 2, OHIO

PLANTS AND SALES OFFICES at Plymouth, Wisc., Chicago, Detroit, Davenport, R.I., Jansburg, N.E.

ABRASIVE DIVISION at Cleveland, Ohio

CANADIAN PLANT: The Cleveland Container, Canada, Ltd., Prescott, Ontario

REPRESENTATIVES

CANADA
METROPOLITAN
NEW YORK
NEW ENGLAND

WM. T. BARRON, EIGHTH LINE, RR #1, OAKVILLE, ONTARIO
E. T. MURRAY, 414 CENTRAL AVE., EAST ORANGE, N.J.
E. P. PACK AND ASSOCIATES, 948 FARMINGTON AVE., WEST HARTFORD, CONN.






STANDARDIZED READY-TO-USE METAL EQUIPMENT

ADAPTABLE FOR EVERY REQUIREMENT

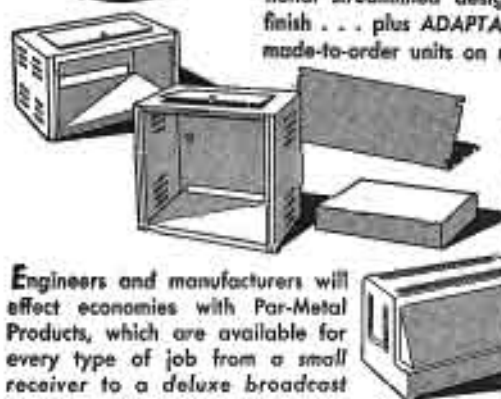Par-Metal Equipment offers many features, including functional streamlined design, rugged construction, beautiful finish . . . plus ADAPTABILITY. Eliminate need for special made-to-order units on many jobs.



Engineers and manufacturers will effect economies with Par-Metal Products, which are available for every type of job from a small receiver to a deluxe broadcast transmitter.

Professional techniques and years of specialization are reflected in the high quality of Par-Metal.

**CABINETS • CHASSIS
PANELS • RACKS**

Write for Catalog



The Industry Offers

BILEY FREQUENCY STANDARD


A frequency standard, employing a 100-ke crystal, has been announced by the Biley Electric Company, Erie, Pennsylvania.

Features a 24-hour frequency stability of two parts in 10 million, when subjected to line voltage fluctuations of as much as 10%. Under adverse conditions of temperature humidity and semi-portable operation the instrument is said to be capable of maintaining an accuracy of two parts in one million for a 30-day period without re-setting.

Frequency source employed is a Biley GT quartz crystal unit temperature stabilized to within 0.1°C in an oven employing a mercury thermostat and external relay.

Long life tubes have been utilized in the crystal oscillator and automatic gain control circuits. Due to operation of the crystals at series resonance, and automatic gain control, the frequency is said to be practically independent of line voltage and circuit component variations; line voltage fluctuation of $\pm 20\%$ causes a frequency change of less than one part per million.

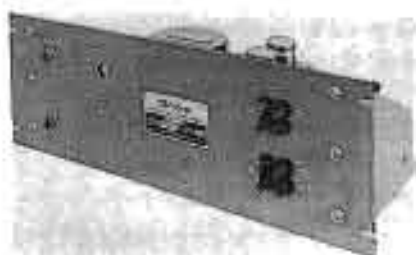Terminals are provided for sine wave or harmonic output at both high impedance and low impedance.



GENERAL RADIO SIGNAL GENERATOR

A general-purpose, amplitude-modulated generator suitable for standard IRE and RMA tests on receivers, type 1001-A, has been announced by the General Radio Co., 275 Massachusetts Ave., Cambridge 38, Mass.

Carrier oscillator in instrument uses a Hartley circuit and is followed by an untuned modulating amplifier. The output voltage is continuously variable by means of a slide-wire calibrated in microvolts and a decade multiplier.

The frequency range is 5 kc to 50 mc, with logarithmic frequency dial and an auxiliary frequency-increment dial.

Output voltage range is 0.1 microvolt to 200 millivolts at the panel jack; 0.05 microvolt to 100 millivolts at the end of a terminated cable.

Output impedance is 10 ohms at panel jack, 50 ohms at end of unterminated cable, or 25 ohms at end of terminated cable.

Internal modulation at 400 cycles up to 80% is provided. External modulation can be used from 20 cycles to 15 kc.

Incidental frequency modulation is below 38 parts per million at 30% modulation.

Stray fields are said to be substantially less than one microvolt per meter at a distance of 2 feet from the generator.



GERTSCH FILTER

An applied acoustics one-half octave filter, model SA-2, has been announced by Gertsch Products, Inc., Los Angeles. Set is composed of separate high and low pass filters having points of 3 db transmission loss ranging from 37.5 to 13,600 cycles ± 2 cycles of 2 per cent, whichever is greater, in one-half octave steps.

HERE'S BIG HELP IN TERMINAL WIRING!

The New JONES FANNING STRIP

Connections are made through Fanning Strip, on bench or anywhere apart from barrier strip, and quickly slipped into assembly.

Use with Jones Barrier Terminal Strips, Nos. 141 and 142, for 1 to 20 terminals.

Simplifies soldering. Insures correct connections. Saves time. Ideal for harness or cable assembly. Brass terminals, cadmium plated. Bakelite mounting. Send for complete data.

The correct wire to correct terminal every time!



9-141 Barrier Strip

9-142 Fanning Strip, Pat. applied for.

HOWARD B. JONES DIVISION
Coch Mfg. Corp.
1026 SOUTH HOMAN AVE. CHICAGO 28, ILL.

BIRTCHE STAINLESS STEEL - LOCKING TYPE

TUBE CLAMPS

Stainless Steel

Corrosion Proof



83 VARIATIONS

Where vibration is a problem, Birtcher Locking TUBE CLAMPS offer a foolproof, practical solution. Recommended for all types of tubes and similar plug-in components.

More than three million of these clamps in use.

FREE CATALOG

Send for samples of Birtcher stainless steel tube clamps and our standard catalog listing tube base types, recommended clamp designs, and price list.

THE BIRTCHE CORPORATION
5087 HUNTINGTON DR. LOS ANGELES 32

AUDIOGRAPH TWO SPEED TAPE RECORDER

A cassette tape recorder, operating at 7½ or 15-inch speeds, by instantaneous switchover, has been announced by Audiograph Co., 1413 El Camino Real, San Carlos, Calif.

Console features a recording amplifier circuit which is said to provide constant-current output from a low impedance source with pre-emphasis equalization, and head interchangeability without response variation.

Three plug-in chassis units, contain recording, playback, and power supplies for the electronic equipment. Amplifier is said to accommodate input levels as low as -10 dbm. Has plug-in tape equalizer. Meter-monitor amplifier provides 0 dbm monitor output and 5 db indication on an meter at normal recording level. A 60-kc oscillator has a calibrated current control for adjustment to various tapes. Playback amplifier is said to provide a peak output of +20 dbm at less than 1% total harmonic distortion which feeds 150 ohm line.

Tape transport mechanism handles 2,400 feet of tape on NAB standard hub, or RMA reels.



SYLVANIA HIGH VACUUM RECTIFIER

A high vacuum rectifier has been announced by the radio division of Sylvania Electric Products Inc., 500 Fifth Avenue, New York 18, N. Y. The tube, lock-in type 7X6, is supplied with a 6.3-volt heater, rated at 1.2 amperes. Has a maximum rated output of 150 milli-amperes. Separate cathode leads.

SPRAGUE HYPASS CAPACITORS

Hypass 3-terminal network feed-through capacitors designed to minimize TV interference from amateur transmitters or attenuate power line-conducted interference from diathermy machines, industrial electronic heating apparatus and other high-frequency signal sources, have been announced by Sprague Products Co., North Adams, Mass.

Units are available in a complete line of capacities and voltages (up to 5,000 volts) for practically any high-frequency filtering requirement.

Bulletin M-432 describing this development in detail will be sent on postcard request.

ELIMAC TRIODE

A triode directly interchangeable with the 592, patterned after the Elmac VT327A radar pulse tube, has been announced by Elmac-McCullough, Inc., 257 San Mateo Ave., San Bruno, Calif.

Tube, a general purpose ray triode, is suitable for both oscillator and power amplifier service. Construction is said to lend itself to power amplifier service at frequencies up to 125 mc.

Plate employs Elmac pyrovac plate material. Non-smitting processed grid material is used.

DUMONT BENT GUN ION TRAP TV TUBES

TV tubes, in the 12½", 15½", 16" and 19" sizes, featuring a bent-gun ion trap, have been announced by the Allen B. DuMont Laboratories, Inc., 2 Main Ave., Passaic, N. J. In bent-gun design the electron and ion beam is aimed by bending the gun so that the ions will be trapped by the anode barrel structure, and the electron beam is then brought to the axis by the action of a single magnetic field.

The bent-gun design is said to permit the production of short neck length tubes, because of the space saved by eliminating the double beam bending magnet, which permits sealing the gun closer to the bulb without restricting neck length for focus and deflecting components.

BRAND-NEW!

- ★ Only two holes in chassis
- ★ Readily-wired lugs
- ★ 19/32" dia. 1½, 2, 2½ and 3" h.
- ★ 10, 15, 20 and 25 w.
- ★ Max. res. 6,000, 9,000, 12,000 and 15,000 ohms



STANDEE-ABOVE-CHASSIS- MOUNTED POWER RESISTOR...

★ Just what the underwriter ordered! Mounts ABOVE chassis. Takes heat out in the open. ½" hole clears terminals below. Mounting bracket takes self-tapping screw.

Wire winding on fibre-glass core, bent in hairpin with mica separator between legs, placed in ceramic tube filled and sealed with cold-setting inorganic cement.

★ Write on business letter-head for literature, sample and quotations.

CLAROSTAT



Controls and Resistors

CLAROSTAT MFG. CO., INC. • DOVER, NEW HAMPSHIRE • In Canada: CANADIAN MARCONI CO., LTD. Montreal, P. Q., and branches

MEASUREMENTS CORPORATION

Peak-to-Peak VOLTMETER

.0005 — 300
VOLTS

MODEL 67

Designed for accurate indication of the peak-to-peak values of symmetrical and asymmetrical waveforms, varying from low frequency square waves to pulses of less than five micro-seconds duration.

.0005-300 volts peak-to-peak, .0002-100 volts r.m.s. in five ranges. Semi-logarithmic, hand calibrated scales.

Provision for connection to 1500 ohm, 1 milliampere graphic recorder or milliammeter.



INPUT IMPEDANCE: 1 megohm shunted by 30 mmfd.

DIMENSIONS: Height 7½", width 7", depth 8½". Weight 8 lbs.

POWER SUPPLY: 117 volts, 50-60 cycles, 35 watts.

MEASUREMENTS CORPORATION
BOONTON NEW JERSEY

AMPERITE

Studio Microphones
at P.A. Prices

Ideal for BROADCASTING

- RECORDING
- PUBLIC ADDRESS

"The ultimate in microphone quality," says Evan Rushing, sound engineer of the Hotel New Yorker.

- Shout right into the new Amperite Microphone—or stand 2 feet away—reproduction is always perfect.
- The only type microphone that is not affected by any climatic conditions.
- Guaranteed to withstand more "knocking around" than any other type mike.

Special Offer: Write for Special Introductory Offer, and 4-page illustrated folder.

AMPERITE Company, Inc.

561 BROADWAY • NEW YORK 12, N. Y.

In Canada: Atlas Radio Corp., Ltd., 560 King St. W., Toronto



Models
RBLG—200 ohms
RRHG—Hi-imp.
List \$42.00



"Contact" Mikes
Model SKH, list \$12.00
Model KKH, list \$18.00

Feedback Amplifier Analysis

(Continued from page 15)

total amount of feedback that may be applied (defined as $20 \log_{10} (1 - A_m \beta)$) is $20 \log_{10} (1 + 100) = 40.1$ db, since 40 db is a voltage ratio of 100 to 1. If a phase margin of 45° against singing is desired (that is, if it were desired to have the magnitude of the phase shift 45° less than 180° at the frequency where $|A \beta|$ is unity) we find that $\phi = 135^\circ$ at a frequency at which $|A \beta|$ is down about 20 db from $A_m \beta$. Thus, $A_m \beta$ can have a maximum value of only 20 db or the db feedback that may be applied in this case is $20 \log_{10} (1 + 10) = 20.8$ db. The value of the voltage divider β may be determined

from the relation $\beta = \frac{A_m \beta}{A_m}$ where A_m is now a voltage ratio.

Circuits for Complex Conditions

In constructing an equivalent circuit for networks that may have somewhat more complicated attenuation-frequency curves, it is sometimes desirable to use slightly more complicated building blocks in the equivalent circuit to reduce the total number of terms that must be added to obtain the phase shift frequency characteristic. Such circuits will suggest themselves in any given situation. One such circuit that is useful in cases where a flat step in the attenuating characteristic is added midway in the high-frequency attenuation curve to reduce the phase shift, is shown in Figure 4. By making use of several identical circuits in cascade with isolation it is, of course, possible to obtain a break from flat to a slope of any multiple of 6 db per octave, and by careful choice of equivalent circuit units most attenuation curves may be closely approximated.

Table I

Tabulation of phase shift against frequency for the example discussed in the text.

ω	$\tan^{-1} \frac{\omega}{\omega'}$	$\tan^{-1} \frac{\omega}{10\omega'}$	$\tan^{-1} \frac{\omega}{1000\omega'}$	ϕ
0.1 ω'	$5^\circ 40'$	$0^\circ 5'$	0°	$-5^\circ 45'$
1 ω'	45°	$5^\circ 40'$	$0^\circ 5'$	$-50^\circ 45'$
10 ω'	$84^\circ 20'$	45°	$5^\circ 40'$	-134°
100 ω'	$89^\circ 20'$	$84^\circ 20'$	45°	$-218^\circ 40'$
1000 ω'	90°	$89^\circ 20'$	$84^\circ 20'$	$-263^\circ 40'$

FREE! Send for it NOW!

**ALLIED'S NEW
1950 CATALOG!**

196 PAGES—
Everything in
Radio and
Electronics



GET RADIO'S
LEADING BUYING GUIDE

Service Technicians and Engineers: ALLIED'S 1950 Buying Guide brings you all the new releases and money-saving values—from the world's largest stocks of test instruments, amplifiers, P.A. systems and equipment, tubes, parts, tools, books and accessories—ready for instant expert shipment. Send today for your FREE new 196-page ALLIED Catalog.

ALLIED RADIO CORP., DEPT. 24-L-9
833 W. Jackson Blvd., Chicago 7, Ill.

☐ Send FREE New ALLIED Catalog.

FREE

Name.....
Address.....

ALLIED RADIO

Here soon-

TV engineering

Watch for
announcement-

TV engineering

For advance
information about

TV engineering

WRITE TO
Bryan Davis Publishing Co., Inc.
52 Vanderbilt Ave., New York, N. Y.

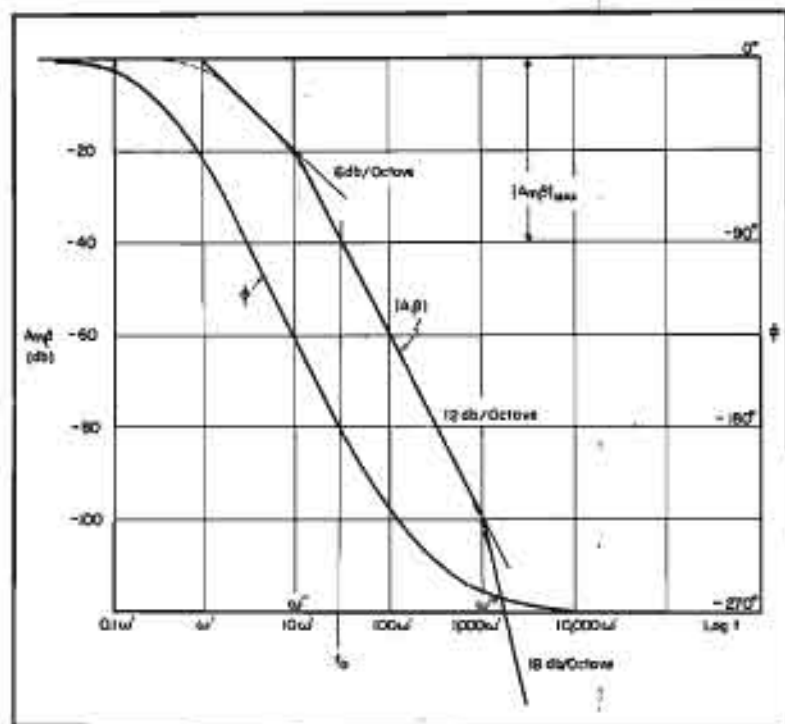


Figure 3
Attenuation and phase shift in the high-frequency region as a function of frequency.

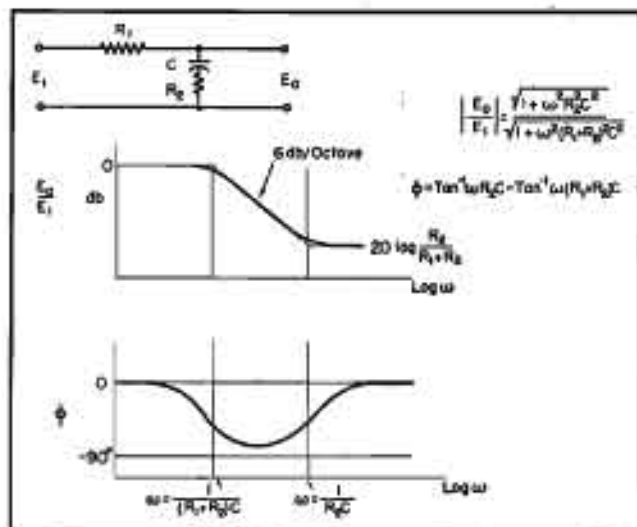


Figure 4
Characteristics of a slightly more complicated equivalent circuit element useful for certain amplifier configurations. For $R_1 = R_2$ slope extends one octave and for $R_1 = R_2$ slope extends one decade.



MOTOROLA CONTROL HEAD
A universal control head, for use with two-way mobile units, has been announced by Motorola Inc., 4545 Augusta Boulevard, Chicago 51, Ill. Unit, features rounded corners and can be mounted in any position on any type of dashboard. Basic unit is said to be adjustable to proper angle, regardless of whether it is mounted on the top, at the center, on the bottom, or any position in between, on dashboard.



Send today for . . .

the only book that covers
the entire field of recording

ELEMENTS OF SOUND RECORDING

By John G. Frayne, Supervisor of Development Engineering; and Halley Wolfe, Development Engineer, both of Electrical Research Products Division, Western Electric Company.

Here is a comprehensive, practical reference volume on basic sound problems for the designer, operating engineer or technician.

The authors discuss in detail those subjects that belong to the restricted field of sound recording and reproduction, and which are not discussed in books devoted to the allied fields of electronics, radio engineering, etc. However, since those interested in studying sound recording have widely different kinds of training and experience, some closely related subjects such as electromechanical analogies, acoustics, vacuum tubes, and audio amplifiers are discussed.

The book includes . . .

A large number of numerical examples to make the design procedure perfectly clear to the reader.

More than 400 diagrams and photographs illustrating every step of the text material.

Contents: Nature of Sound, Sound Waves and their Perception, Electrical, Acoustical, and Mechanical Circuits, Microphones and their Uses, Vacuum Tubes, Audio Amplifiers, Network Theory, Attenuators, Filters, Equalizers, Compression and Limiting, Recording Systems, Electrical Measurements, Principles of Disk Recording, Disk Records and their Processing, Fundamental Principles of Variable-Density Recording, The Light Valve, Variable-Intensity Modulators, Principles of Variable-Area Recording, Variable-Area Modulators, Noise-Reduction Methods, Intermodulation Test Methods, Flutter and its Measurement, Film and Disk Drive Mechanisms, Motor Drive Systems, Film Laboratory Processes, Recording, 35-mm Motion Picture Recording Systems, 16-mm Sound Film Systems, Acoustics of Stages and Theatres, Stereophonic Recording.

1949

666 pages

483 illus.

\$8.50

10-DAY
EXAMINATION



ON APPROVAL COUPON
JOHN WILEY & SONS, INC.
440 Fourth Ave., New York 16, N. Y.
Please send me, on 10 days' approval, a copy of Frayne and Wolfe's **ELEMENTS OF SOUND RECORDING**. If I decide to keep the book, I will remit \$8.50 plus postage; otherwise, I will return the book postpaid.

Name
Address
City Zone State
Employed by
(Offer not valid outside U.S.) C-11-49



TYPE
BH6



TYPE
TCO-1
OPER. TEMP. 75°C.
RATING 6.3V. - 5.5W

But A COMPLETE
KNOWLEDGE OF
FREQUENCY CONTROL

Type BH6 . . . Miniature size crystal unit. Frequency range . . . 1 MC to 100 MC . . . Tolerances meet all commercial or military specifications . . . hermetically sealed . . . in demand where space limitations are a problem . . . precision performance based on Bliley's complete knowledge of frequency control applications.

Type TCO-1 . . . Temperature control oven . . . for performance $\pm .0001\%$ between -55°C and $+70^{\circ}\text{C}$. . . specify BH6 crystal units with TCO-1 temperature control ovens. (For dual units specify TCO-2). Precision performance based on Bliley's complete knowledge of temperature control ovens.

*** "First . . . For 20 Years"**
Bliley
CRYSTALS
BILLEY ELECTRIC COMPANY
UNION STATION BLDG., ERIE, PA.

Last Minute Reports . . .

ACTIVITY IN THE HIGH FREQUENCIES has accelerated demand for very thin quartz crystal oscillator plates, having fundamental frequencies up to 100 mc or even higher, and prompted development of unusual grinding methods and machinery. In the course of an investigation of this problem, L. T. Sogn and W. J. Howard of the National Bureau of Standards designed equipment capable of producing .001" thick plates with a high degree of parallelism and flatness. . . . Effective November 1, the letter U will supplement the N or W now being used in the radio propagation broadcasts from WWV, U referring to unstable conditions. . . . John D. Kraus has been appointed Professor of Electrical Engineering at Ohio State University. . . . A 150-kw transmitter, developed by RCA, is now in operation in Munich, Germany, carrying the Voice of America programs. . . . WXEL, owned by the Empire Coil Co., will soon begin operation in Cleveland on channel nine. They will use a G. E. 3-kw transmitter and a 6-bay antenna mounted atop a 438' tower. Tom Friedman is chief engineer. . . . Dr. Martin D. Freundlich is now with Airborne Instruments Laboratory, Mineola, New York, in charge of the tube laboratory in the applied physics section which is directed by Rodney F. Simon.

. . . Russel O. Hudson is now vice president in charge of sales of the Audio and Video Products Corp., 1650 Broadway, N. Y. C., and W. Oliver Summerlin has been named vice president in charge of engineering. . . . WGKV now has a 3-kw FM transmitter operating at 98.5 mc. . . . WHAS-TV, Louisville, Kentucky, will soon install a 12-bay antenna developed by G. E. Picture and sound signals will radiate from forty-eight batwing-shaped elements spaced in groups of four approximately every six feet along the antenna mast. . . . A. E. Bennett, formerly chief engineer at Hoffman Radio, is now chief engineer and general manager of Audio-graph Company, San Carlos, California.

. . . Dr. Frank B. Jewett, formerly president of the Bell Telephone Laboratories, will receive the 1950 medal of the National Research Institute, Inc. . . . The Pennsylvania Electric Company have installed a microwave system to provide communications over a ten-mile air line between sub-station points. . . . Dr. Cleo Brunetti, formerly with the Bureau of Standards and now associate director at the Stanford Research Institute, is now on a tour in Europe, visiting the Admiralty Research Laboratory at Teddington and the Royal Aircraft Establishment at Farnborough, in England. . . . The Graybar Electric Company has announced that it will distribute a complete line of Altec Lansing sound products. Graybar will continue to sell the present inventory of Western Electric sound products, which were recently transferred from Western Electric to Altec Lansing. . . . Frank B. Powers, formerly assistant vice president of the American Car and Foundry Company, has been appointed director of manufacturing operations of Federal Telephone and Radio Corporation. . . . The second issue of the Hewlett-Packard journal has been published with a paper on a new frequency standard and time interval generator. . . . The General Radio Company, 275 Massachusetts Ave., Cambridge 39, Mass., have released a four-page folder illustrating the complete line of variacs.



for
**POLICE,
TAXICAB,
PUBLIC-UTILITY**



radio communication systems, the Micrometer Frequency Meter will monitor one or a dozen transmitters, on any frequencies up to 175 mc., with accuracy 0.005%. Four models, priced \$129.00 to \$202.00, net. Immediate delivery.

— wire or write today —

**LAMPKIN
LABORATORIES, Inc.**
Bradenton . . . Florida

ADVERTISERS IN THIS ISSUE COMMUNICATIONS INDEX NOVEMBER, 1949


ALLIED RADIO CORP.	31
Agency: George Brudis, Advertising	
AMPERITE CO.	30
Agency: R. J. Gold Co.	
BELL TELEPHONE LABORATORIES	1
Agency: N. W. Ayer & Son, Inc.	
BIRCHER CORP.	28
Agency: W. C. Jeffries Co.	
BILLEY ELECTRIC CO.	32
Agency: John Harder, Postmaster	
J. H. BUNNELL & CO.	Inside Front Cover
Agency: J. H. Bunnell	
CLARISTAT MFG. CO., INC.	29
Agency: Austin C. Leachman & Staff	
THE CLEVELAND CONTAINER CO.	27
Agency: The Health Service Co.	
ALLEN D. DUMONT LABORATORIES, INC.	0
Agency: Austin C. Leachman & Staff	
GENERAL ELECTRIC CO.	4, 9
Agency: Maxon, Inc.	
GENERAL RADIO CO.	Inside Back Cover
Agency: The Radio Press	
HEWLETT-PACKARD CO.	Back Cover
Agency: L. C. Cole, Advertising	
INSULINE CORPORATION OF AMERICA	26
Agency: Deas & Co., Inc.	
HOWARD B. JONES DIV. CINCH MFG. CORP.	28
Agency: Brundis, MacKenzie & Co.	
KELLOGG SWITCHBOARD & SUPPLY CO.	3
Agency: Glenn Jordan, Stouffer, Tex.	
LAMPKIN LABORATORIES, INC.	32
NACHLETT LABORATORIES, INC.	18
Agency: E. Scott Brown, Advertising	
MEASUREMENTS CORPORATION	29
Agency: Frederick Brink	
JAMES MILLER MFG. CO., INC.	24
PAR-METAL PRODUCTS CORP.	25
Agency: R. J. Gold Co.	
RADIO CORPORATION OF AMERICA	16, 17
Agency: J. Walter Thompson Co.	
WARD LEONARD ELECTRIC CO.	22
Agency: Henry E. Zollic, Advertising	
JOHN WILEY & SONS, INC.	31
Agency: The Watson Co.	

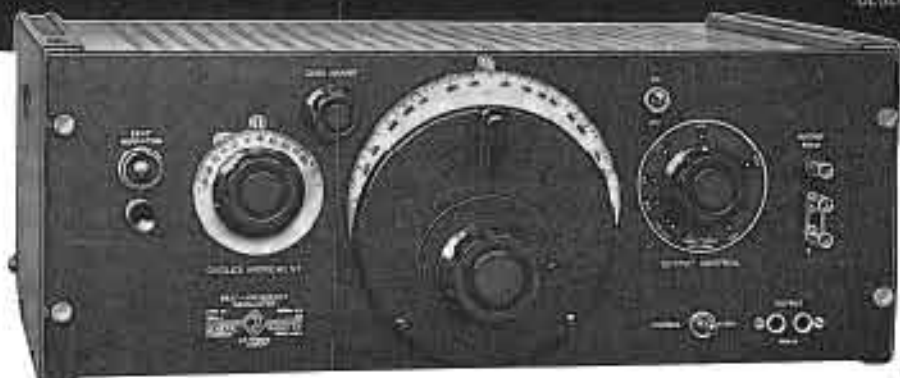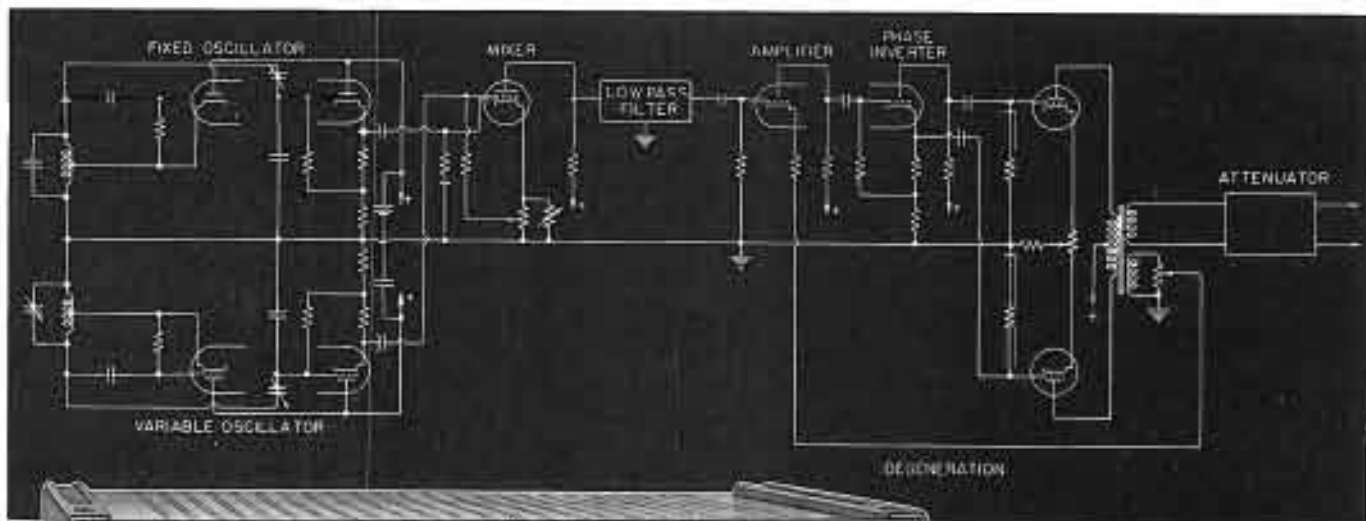

**USE THIS OSCILLATOR FOR GREATER
ACCURACY • LESS DISTORTION •
IMPROVED ZERO ADJUSTMENT •
MANY OPERATING CONVENIENCES**

The popularity of the G-R TYPE 1304-A Beat Frequency Oscillator is due to these features:

- **FREQUENCY RANGE:** 20 to 20,000 cycles
- **FREQUENCY CALIBRATION:** can be standardized within 1 cycle at any time by setting instrument to line frequency or zero beat.
- **LOW DISTORTION:** harmonic content approximately 0.25% between 100 and 7500 cycles with 0.3 watt maximum output; on HIGH OUTPUT of 1 watt, distortion less than 1% between 100 and 7500 cycles. Below 100 and above 7500 cycles distortion is higher.
- **ZERO BEAT INDICATOR:** neon lamp for zero beat at line frequency or zero scale.
- **FREQUENCY STABILITY:** drift from cold start less than 7 cycles in first hour and completed in 2 hours.
- **OUTPUT IMPEDANCE:** 600 ohms, either grounded or balanced-to-ground, and essentially constant at all output voltages.
- **OUTPUT VOLTAGE:** approximately 25 volts open circuit. For matched resistive load voltage varies less than ± 0.25 db between 20 and 20,000 cycles.
- **OUTPUT CONTROL:** calibrated from +25 db to -20 db referred to 1 milliwatt into 600 ohms.

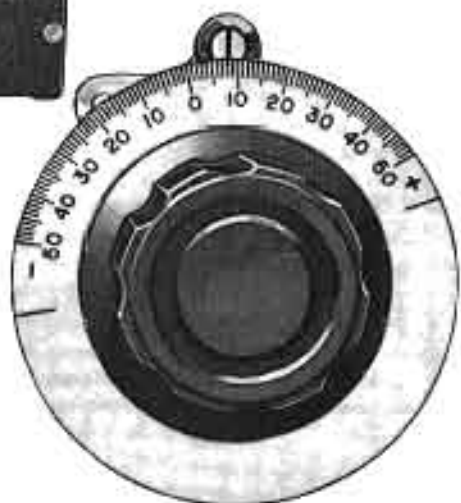

The frequency-increment dial, calibrated from +50 to -50 cycles is a great convenience. The main dial is engraved from 20 to 20,000 cycles with a true logarithmic scale; the calibration is accurate within $\pm(1\% + 0.5 \text{ cycle})$. The total scale length is 12 inches over an angle of rotation of 240° . This dial can be coupled to a recorder to record frequency characteristics.

TYPE 1304-A BEAT-FREQUENCY OSCILLATOR \$450.00

WRITE FOR COMPLETE DATA




GENERAL RADIO COMPANY

Cambridge 39, Massachusetts

90 West St., New York 6 920 S. Michigan Ave., Chicago 5 1000 N. Seward St., Los Angeles 38



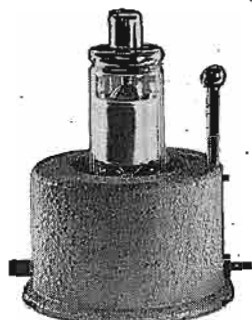NEW *-hp-* ACCESSORIES INCREASE SCOPE OF YOUR *-hp-* VOLTMETERS



-hp- 452A Capacitive Voltage Divider

For *-hp-* 400A, 400C and 410A Voltmeters. Safely measure power, supersonic and dielectric heating voltages to 25 kv. Accuracy $\pm 3\%$. Frequency range, 25 cps to 20 mc. Division ratio 1,000:1. Input capacity 15 μf . Price \$75.00.





-hp- 453A Capacitive Voltage Divider

For *-hp-* 410A Voltmeter. Increases range so transmitter voltages can be measured quickly, easily. Accuracy $\pm 1\%$. Division ratio, 100:1. Input capacity approx. 2 μf . Max. voltage 2,000 v. For frequencies 10 kc and above. Price \$20.00.

-hp- 454A Capacitive Voltage Divider

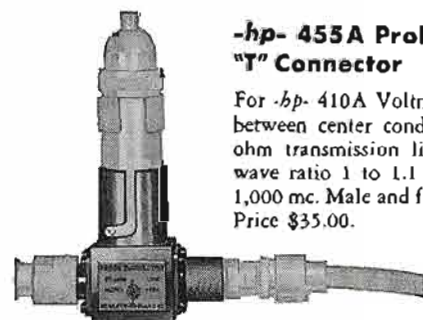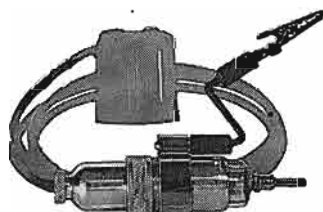For *-hp-* 400C Voltmeters. Safely measure power, audio, supersonic and rf voltages. Accuracy $\pm 3\%$. Division ratio, 100:1. Input impedance 50 megohms, resistive shunted with 2.75 μf capacity. Max. voltage, 1,500 v. Price \$20.00.



-hp- 455A Probe Coaxial "T" Connector


For *-hp-* 410A Voltmeter. Measures voltages between center conductor and sheath of 50 ohm transmission line. Maximum standing wave ratio 1 to 1.1 at 500 mc; 1 to 1.2 at 1,000 mc. Male and female Type "N" fittings. Price \$35.00.

Extend the usefulness of your present *-hp-* voltmeters with these new precision-built *-hp-* accessories. Save time and work. Simplify tedious jobs. Make fast, accurate measurements far beyond the original range of your instruments.

-hp- 470A-470F Shunt Resistors

For *-hp-* 400A or 400C Voltmeters, to measure currents as small as 1 μa full scale. Accuracy, $\pm 1\%$ to 100 kc, $\pm 5\%$ to 2 mc. Max. power dissipation 1 watt.

Instrument	Value	Price
<i>-hp-</i> 470A	0.1 Ω	\$7.50
<i>-hp-</i> 470B	1.0 Ω	6.00
<i>-hp-</i> 470C	10.0 Ω	6.00
<i>-hp-</i> 470D	100 Ω	6.00
<i>-hp-</i> 470E	600 Ω	6.00
<i>-hp-</i> 470F	1,000 Ω	6.00

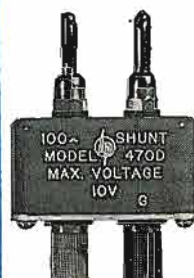

-hp- 459A DC Resistive Voltage Multiplier

For *-hp-* 410A Voltmeter. Gives maximum safety and convenience for measuring high voltages as in television receivers, etc. Accuracy $\pm 5\%$. Multiplication ratio 100:1. Input impedance 12,000 megohms. Max. voltage 30 kv. Max. current drain 2.5 microamperes. Price \$20.00.



-hp- 458A Probe Coaxial "N" Connector

For *-hp-* 410A Voltmeter. Measures volts at open end of 50 ohm transmission line. (No terminating resistor). Uses female Type "N" fitting. Price \$17.50.

*All prices and data subject to change
Prices F. O. B. Palo Alto*

Write for details or see your *-hp-* Representative.

HEWLETT-PACKARD CO.

1935E PAGE MILL ROAD • PALO ALTO, CALIFORNIA

Export Agents: Frazer & Hanson, Ltd.

301 Clay Street, San Francisco 11, California, U.S.A.

hp laboratory instruments
FOR SPEED AND ACCURACY